



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Logic Minimization, K-Maps - 1

Reetinder Sidhu

Department of Computer Science and Engineering

DIGITAL DESIGN AND COMPUTER ORGANIZATION

Logic Minimization, K-Maps - 1

Reetinder Sidhu

Department of Computer Science and
Engineering

- Digital Design
 - ▶ Combinational logic design
 - ★ **Logic Minimization, K-Maps - 1**
 - ▶ Sequential logic design
- Computer Organization
 - ▶ Architecture (microprocessor instruction set)
 - ▶ Microarchitecture (microprocessor operation)

Concepts covered

- Boolean Formula Terminology
- Sum of Products and Product of Sums standard forms
- Truth Table to Boolean Formula / Logic Circuit
- Logic Minimization using Boolean Identities



From Truth Table to Boolean Formula and its Minimization

- Given a combinational logic circuit or Boolean formula, we have learnt to construct its truth table
- But, given a truth table, how to construct a Boolean formula (or combinational logic circuit) for it?
- Also, as there are multiple Boolean formulas / logic circuits for each truth table, how to pick the minimal one?
- Above problem is called **logic minimization**
 - ▶ many metrics: smallest, fastest, least power consumption
 - ▶ our metric: smallest two level Sum of Products formula
 - ▶ may be more than one solution

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula Terminology

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula Terminology



- **Literal** Boolean variable or its complement (ex: \bar{c})

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula Terminology

- **Literal** Boolean variable or its complement (ex: \bar{c})
- **Product (or implicant)** AND of two or more literals (ex: $ab\bar{c}$)

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula Terminology



- **Literal** Boolean variable or its complement (ex: \bar{c})
- **Product (or implicant)** AND of two or more literals (ex: $ab\bar{c}$)
- **Minterm** Product involving all inputs to Boolean function

- **Literal** Boolean variable or its complement (ex: \bar{c})
- **Product (or implicant)** AND of two or more literals (ex: $ab\bar{c}$)
- **Minterm** Product involving all inputs to Boolean function

a	b	c	minterm	name
0	0	0	$\bar{a}\bar{b}\bar{c}$	m_0
0	0	1	$\bar{a}\bar{b}c$	m_1
0	1	0	$\bar{a}b\bar{c}$	m_2
0	1	1	$\bar{a}bc$	m_3
1	0	0	$a\bar{b}\bar{c}$	m_4
1	0	1	$a\bar{b}c$	m_5
1	1	0	$ab\bar{c}$	m_6
1	1	1	abc	m_7

Minterms for three inputs a , b and c

- **Literal** Boolean variable or its complement (ex: \bar{c})
- **Product (or implicant)** AND of two or more literals (ex: $ab\bar{c}$)
- **Sum** OR of two or more literals
- **Minterm** Product involving all inputs to Boolean function

<i>a</i>	<i>b</i>	<i>c</i>	minterm	name
0	0	0	$\bar{a}\bar{b}\bar{c}$	m_0
0	0	1	$\bar{a}\bar{b}c$	m_1
0	1	0	$\bar{a}b\bar{c}$	m_2
0	1	1	$\bar{a}bc$	m_3
1	0	0	$a\bar{b}\bar{c}$	m_4
1	0	1	$a\bar{b}c$	m_5
1	1	0	$ab\bar{c}$	m_6
1	1	1	abc	m_7

Minterms for three inputs a , b and c

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula Terminology

- **Literal** Boolean variable or its complement (ex: \bar{c})
- **Product (or implicant)** AND of two or more literals (ex: $ab\bar{c}$)
- **Minterm** Product involving all inputs to Boolean function
- **Sum** OR of two or more literals
- **Maxterm** Sum involving all inputs to Boolean function

<i>a</i>	<i>b</i>	<i>c</i>	minterm	name
0	0	0	$\bar{a}\bar{b}\bar{c}$	m_0
0	0	1	$\bar{a}\bar{b}c$	m_1
0	1	0	$\bar{a}b\bar{c}$	m_2
0	1	1	$\bar{a}bc$	m_3
1	0	0	$a\bar{b}\bar{c}$	m_4
1	0	1	$a\bar{b}c$	m_5
1	1	0	$ab\bar{c}$	m_6
1	1	1	abc	m_7

Minterms for three inputs a , b and c

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula Terminology

- **Literal** Boolean variable or its complement (ex: \bar{c})
- **Product (or implicant)** AND of two or more literals (ex: $ab\bar{c}$)
- **Minterm** Product involving all inputs to Boolean function

<i>a</i>	<i>b</i>	<i>c</i>	minterm	name
0	0	0	$\bar{a}\bar{b}\bar{c}$	m_0
0	0	1	$\bar{a}\bar{b}c$	m_1
0	1	0	$\bar{a}b\bar{c}$	m_2
0	1	1	$\bar{a}bc$	m_3
1	0	0	$a\bar{b}\bar{c}$	m_4
1	0	1	$a\bar{b}c$	m_5
1	1	0	$ab\bar{c}$	m_6
1	1	1	abc	m_7

Minterms for three inputs a , b and c

- **Sum** OR of two or more literals
- **Maxterm** Sum involving all inputs to Boolean function

<i>a</i>	<i>b</i>	<i>c</i>	maxterm	name
0	0	0	$a + b + c$	M_0
0	0	1	$a + b + \bar{c}$	M_1
0	1	0	$a + \bar{b} + c$	M_2
0	1	1	$a + \bar{b} + \bar{c}$	M_3
1	0	0	$\bar{a} + b + c$	M_4
1	0	1	$\bar{a} + b + \bar{c}$	M_5
1	1	0	$\bar{a} + \bar{b} + c$	M_6
1	1	1	$\bar{a} + \bar{b} + \bar{c}$	M_7

Maxterms for three inputs a , b and c

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Sum of Products (SOP)

SOP Form

Sum of all minterms corresponding to a 1 output

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Sum of Products (SOP)

SOP Form

Sum of all minterms corresponding to a 1 output

SOP Example

- Truth table:

<i>a</i>	<i>b</i>	<i>c</i>	<i>y</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Sum of Products (SOP)

SOP Form

Sum of all minterms corresponding to a 1 output

SOP Example

- Truth table:

<i>a</i>	<i>b</i>	<i>c</i>	<i>y</i>	minterm	name
0	0	0	0	$\overline{a}\overline{b}\overline{c}$	m_0
0	0	1	0	$\overline{a}\overline{b}c$	m_1
0	1	0	0	$\overline{a}b\overline{c}$	m_2
0	1	1	1	$\overline{a}bc$	m_3
1	0	0	1	$a\overline{b}\overline{c}$	m_4
1	0	1	0	$a\overline{b}c$	m_5
1	1	0	1	$ab\overline{c}$	m_6
1	1	1	1	abc	m_7

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Sum of Products (SOP)

SOP Form

Sum of all minterms corresponding to a 1 output

SOP Example

- Truth table:

a	b	c	y	minterm	name
0	0	0	0	$\bar{a}\bar{b}\bar{c}$	m_0
0	0	1	0	$\bar{a}\bar{b}c$	m_1
0	1	0	0	$\bar{a}b\bar{c}$	m_2
0	1	1	1	$\bar{a}bc$	m_3
1	0	0	1	$a\bar{b}\bar{c}$	m_4
1	0	1	0	abc	m_5
1	1	0	1	$ab\bar{c}$	m_6
1	1	1	1	abc	m_7

- SOP form Boolean formula:

$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$
$$y = m_3 + m_4 + m_6 + m_7$$

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Sum of Products (SOP)

SOP Form

Sum of all minterms corresponding to a 1 output

SOP Example

- Truth table:

a	b	c	y	minterm	name
0	0	0	0	$\bar{a}\bar{b}\bar{c}$	m_0
0	0	1	0	$\bar{a}\bar{b}c$	m_1
0	1	0	0	$\bar{a}b\bar{c}$	m_2
0	1	1	1	$\bar{a}bc$	m_3
1	0	0	1	$a\bar{b}\bar{c}$	m_4
1	0	1	0	$a\bar{b}c$	m_5
1	1	0	1	$ab\bar{c}$	m_6
1	1	1	1	abc	m_7

- SOP form Boolean formula:

$$y = \bar{a}bc + \bar{a}\bar{b}c + ab\bar{c} + abc$$
$$y = m_3 + m_4 + m_6 + m_7$$

- Sigma (Σ) notation:

$$y = \Sigma(m_3, m_4, m_6, m_7)$$
$$y = \Sigma(3, 4, 6, 7)$$

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Sum of Products (SOP)

SOP Form

Sum of all minterms corresponding to a 1 output

SOP Example

- Truth table:

a	b	c	y	minterm	name
0	0	0	0	$\bar{a}\bar{b}\bar{c}$	m_0
0	0	1	0	$\bar{a}\bar{b}c$	m_1
0	1	0	0	$\bar{a}b\bar{c}$	m_2
0	1	1	1	$\bar{a}bc$	m_3
1	0	0	1	$a\bar{b}\bar{c}$	m_4
1	0	1	0	abc	m_5
1	1	0	1	$ab\bar{c}$	m_6
1	1	1	1	abc	m_7

- SOP form Boolean formula:

$$y = \bar{a}bc + \bar{a}\bar{b}c + ab\bar{c} + abc$$
$$y = m_3 + m_4 + m_6 + m_7$$

- Sigma (Σ) notation:

$$y = \Sigma(m_3, m_4, m_6, m_7)$$
$$y = \Sigma(3, 4, 6, 7)$$

- If the Boolean function is called f :

$$y = f(a, b, c)$$

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Products of Sum (POS)

POS Form

Product of all maxterms corresponding to a 0 output

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Products of Sum (POS)

POS Form

Product of all maxterms corresponding to a 0 output

POS Example

- Truth table:

<i>a</i>	<i>b</i>	<i>c</i>	<i>y</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Products of Sum (POS)

POS Form

Product of all maxterms corresponding to a 0 output

POS Example

- Truth table:

<i>a</i>	<i>b</i>	<i>c</i>	<i>y</i>	maxterm	name
0	0	0	0	$a + b + c$	M_0
0	0	1	0	$a + b + \bar{c}$	M_1
0	1	0	0	$a + \bar{b} + c$	M_2
0	1	1	1	$a + \bar{b} + \bar{c}$	M_3
1	0	0	1	$\bar{a} + b + c$	M_4
1	0	1	0	$\bar{a} + b + \bar{c}$	M_5
1	1	0	1	$\bar{a} + \bar{b} + c$	M_6
1	1	1	1	$\bar{a} + \bar{b} + \bar{c}$	M_7

LOGIC MINIMIZATION, K-MAPS - 1

Boolean Formula using Products of Sum (POS)

POS Form

Product of all maxterms corresponding to a 0 output

POS Example

- Truth table:

<i>a</i>	<i>b</i>	<i>c</i>	<i>y</i>	maxterm	name
0	0	0	0	$a + b + c$	M_0
0	0	1	0	$a + b + \bar{c}$	M_1
0	1	0	0	$a + \bar{b} + c$	M_2
0	1	1	1	$a + \bar{b} + \bar{c}$	M_3
1	0	0	1	$\bar{a} + b + c$	M_4
1	0	1	0	$\bar{a} + b + \bar{c}$	M_5
1	1	0	1	$\bar{a} + \bar{b} + c$	M_6
1	1	1	1	$\bar{a} + \bar{b} + \bar{c}$	M_7

- SOP form Boolean formula:

$$y = (a + b + c)(a + b + \bar{c})(\bar{a} + b + c)(\bar{a} + b + \bar{c})$$
$$y = M_0 M_1 M_2 M_5$$

POS Form

Product of all maxterms corresponding to a 0 output

POS Example

- Truth table:

<i>a</i>	<i>b</i>	<i>c</i>	<i>y</i>	maxterm	name
0	0	0	0	$a + b + c$	M_0
0	0	1	0	$a + b + \bar{c}$	M_1
0	1	0	0	$a + \bar{b} + c$	M_2
0	1	1	1	$a + \bar{b} + \bar{c}$	M_3
1	0	0	1	$\bar{a} + b + c$	M_4
1	0	1	0	$\bar{a} + b + \bar{c}$	M_5
1	1	0	1	$\bar{a} + \bar{b} + c$	M_6
1	1	1	1	$\bar{a} + \bar{b} + \bar{c}$	M_7

- SOP form Boolean formula:

$$y = (a + b + c)(a + b + \bar{c})(\bar{a} + b + c)(\bar{a} + b + \bar{c})$$
$$y = M_0 M_1 M_2 M_5$$

- Pi (Π) notation:

$$y = \Pi(M_0, M_1, M_2, M_5)$$

$$y = \Pi(0, 1, 2, 5)$$

POS Form

Product of all maxterms corresponding to a 0 output

POS Example

- Truth table:

<i>a</i>	<i>b</i>	<i>c</i>	<i>y</i>	maxterm	name
0	0	0	0	$a + b + c$	M_0
0	0	1	0	$a + b + \bar{c}$	M_1
0	1	0	0	$a + \bar{b} + c$	M_2
0	1	1	1	$a + \bar{b} + \bar{c}$	M_3
1	0	0	1	$\bar{a} + b + c$	M_4
1	0	1	0	$\bar{a} + b + \bar{c}$	M_5
1	1	0	1	$\bar{a} + \bar{b} + c$	M_6
1	1	1	1	$\bar{a} + \bar{b} + \bar{c}$	M_7

- SOP form Boolean formula:

$$y = (a + b + c)(a + b + \bar{c})(\bar{a} + b + c)(\bar{a} + b + \bar{c})$$
$$y = M_0 M_1 M_2 M_5$$

- Pi (Π) notation:

$$y = \Pi(M_0, M_1, M_2, M_5)$$

$$y = \Pi(0, 1, 2, 5)$$

- If the Boolean function is called f :

$$y = f(a, b, c)$$

Logic Minimization Example

① Minimize:

$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

Logic Minimization Example

① Minimize:

$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

② Using distributive law:

$$y = bc(\bar{a} + a) + a\bar{c}(b + \bar{b})$$

Logic Minimization Example

- ① Minimize:
$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$
- ② Using distributive law:
$$y = bc(\bar{a} + a) + a\bar{c}(b + \bar{b})$$
- ③ Using complement law:
$$y = bc(1) + a\bar{c}(1)$$

Logic Minimization Example


- ① Minimize:
$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$
- ② Using distributive law:
$$y = bc(\bar{a} + a) + a\bar{c}(b + \bar{b})$$
- ③ Using complement law:
$$y = bc(1) + a\bar{c}(1)$$
- ④ Using identity law:
$$y = bc + a\bar{c}$$

Logic Minimization Example

- ① Minimize:
$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$
- ② Using distributive law:
$$y = bc(\bar{a} + a) + a\bar{c}(b + \bar{b})$$
- ③ Using complement law:
$$y = bc(1) + a\bar{c}(1)$$
- ④ Using identity law:
$$y = bc + a\bar{c}$$

The three representations below are different ways of specifying **the same Boolean function**:

$$a \cdot \bar{c} + b \cdot c$$

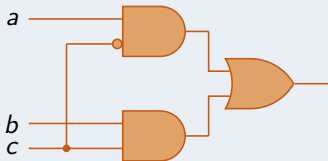

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

LOGIC MINIMIZATION, K-MAPS - 1

Think About It



Think About It

Logic Circuit Example

- Draw the logic circuit diagram for:
$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

LOGIC MINIMIZATION, K-MAPS - 1



Think About It

Logic Circuit Example

- Draw the logic circuit diagram for:
$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

Equivalence Example

- Prove that:
$$bc + a\bar{c} + ab = bc + a\bar{c}$$

Think About It

Logic Circuit Example

- Draw the logic circuit diagram for:
 $y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$

Equivalence Example

- Prove that:
 $bc + a\bar{c} + ab = bc + a\bar{c}$
▶ Hint: $bc + a\bar{c} + ab(c + \bar{c})$

Think About It

Logic Circuit Example

- Draw the logic circuit diagram for:
$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

Equivalence Example

- Prove that:
$$bc + a\bar{c} + ab = bc + a\bar{c}$$

► Hint: $bc + a\bar{c} + ab(c + \bar{c})$

Minimization Example

- Minimize:
$$y = (a + b + c)(a + b + \bar{c})(a + \bar{b} + c)(\bar{a} + b + \bar{c})$$

Think About It

Logic Circuit Example

- Draw the logic circuit diagram for:
$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

Equivalence Example

- Prove that:
$$bc + a\bar{c} + ab = bc + a\bar{c}$$

► Hint: $bc + a\bar{c} + ab(c + \bar{c})$

Minimization Example

- Minimize:
$$y = (a + b + c)(a + b + \bar{c})(a + \bar{b} + c)(\bar{a} + b + \bar{c})$$

► Hint:

$$y = (a(a + b + \bar{c}) + b(a + b + \bar{c}) + c(a + b + \bar{c}))(a(\bar{a} + b + \bar{c}) + \bar{b}(\bar{a} + b + \bar{c}) + c(\bar{a} + b + \bar{c}))$$