

2 Marks Questions:

1. Construct the logic circuit of a 2:1 mux using only two input NAND gates. How many gates are required? Briefly justify your answer.

Solution:

Function Table:

Selection Input (s)	Output
0	A
1	B

- A and B are data input lines


Equation

$$Y = (s' A + s B)$$

With NAND gates

$$Y = ((s'A)'(sB)')' = ((s' A)' (s B)')'$$

Circuit Diagram

 


Number of NAND gates required are 3+1(to complement S)

2: Implement NOT gate, AND gate, and OR gate using 2:1 MUX. Show the truth table.

Solution:


Implementation of NOT gate

 

Truth Table

x	f
0	1
1	0


Implementation of AND gate:

 

Truth Table

x	y	f	$f \rightarrow y$
0	0	0	$f = 0$
0	1	0	
1	0	0	$f = y$
1	1	1	

Implementation of OR Gate

 


Truth Table

x	y	f	$f \rightarrow y$
0	0	0	$f = y$
0	1	1	
1	0	1	$f = 1$
1	1	1	

3: Implement Decoder for the equation $f(x, y, z) = \sum(1, 2, 4, 7)$

Solution:

x	y	z	Output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

4: List few comparison of Combinational logic circuit and sequential Logic Circuit

Solution:

Combinational Logic Circuit

- It has one or more inputs and one or more outputs.
- Its output is determined by the present values of inputs only.
- It does not have a memory.
- It does not have a feedback path.
- Its operation can be described by the truth table.

- It does not have a clock signal.
- It does not depend upon clock transition.
- The circuit is more simpler.
- It is built using basic gates like, NOT, NAND, AND , OR etc
- Its examples are subtractor, adders, Multiplexers and demultiplexers.


Sequential Logic Circuit :

- It has one or more inputs and one or more outputs.
- Its output is determined by the present values of input as well as the past values of output.
- It has a memory
- It has a feedback path
- Its operation can be described by truth table and timing diagram
- It may be or may not have a clock signal.
- Its action is governed by clock transition
- The circuit is more complex
- It is built using basic gates and combinational gates.
- Its examples include flip flops , shift registers.


5: Given the input waveforms shown in [Figure](#) , sketch the output, Q, of an SR latch.




Solution:

 

 6. Write the transition conditions for w at the arrows in the state diagram.




Solution:

 

6 Marks


1: Implement MUX for the following equation $F(x, y) = \sum(0, 1, 3)$

Solution:

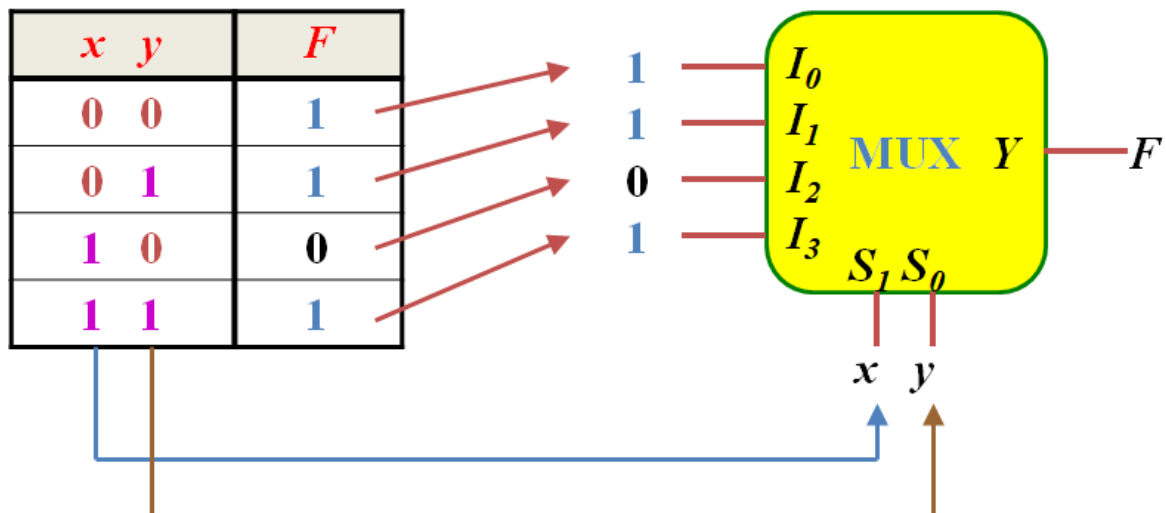

2: Implement MUX for the equation $F(x, y, z) = \sum(1, 2, 6, 7)$


Solution:

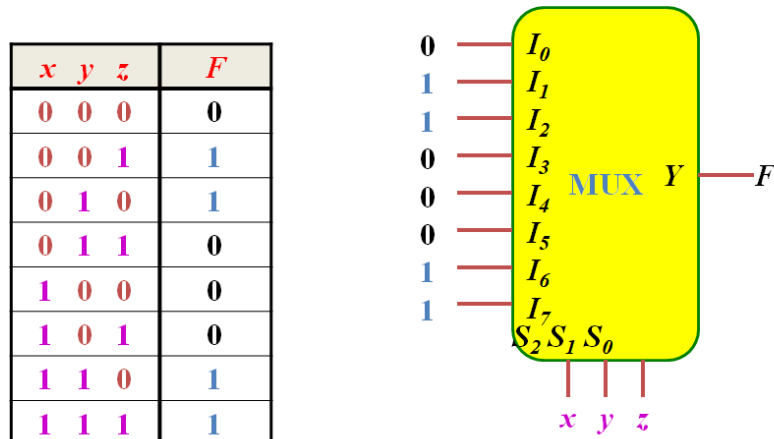

3: Construct 8:1 MUX using two 4:1 MUX and one 2:1 MUX


Solution:

- 8-to-1 MUX using Dual 4-to-1 MUX

 


4: Design 4:16 decoder using two 3:2 decoder

Solution:

 

 5: Write a minimized Boolean equation for the function performed by the circuit



Solution:

$$Y = A + \overline{C \oplus D} = A + CD + \overline{C}\overline{D}$$