



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Counters - 1

Reetinder Sidhu

Department of Computer Science and Engineering

DIGITAL DESIGN AND COMPUTER ORGANIZATION

Counters - 1

Reetinder Sidhu

Department of Computer Science and
Engineering

COUNTERS - 1

Course Outline

- Digital Design
 - ▶ Combinational logic design
 - ▶ Sequential logic design
 - ★ **Counters - 1**
- Computer Organization
 - ▶ Architecture (microprocessor instruction set)
 - ▶ Microarchitecture (microprocessor operation)

Concepts covered

- Counters

COUNTERS - 1

Motivation



COUNTERS - 1

Motivation



- How does the timer/stopwatch app on your mobile work?

COUNTERS - 1

Motivation




- How does the timer/stopwatch app on your mobile work?
- The clock period of a 2GHz processor is 0.5 ns

- How does the timer/stopwatch app on your mobile work?
- The clock period of a 2GHz processor is 0.5 ns
- Need a way to count clock periods based on which time intervals such as microseconds, seconds etc. can be measured


COUNTERS - 1

Counters

- Counter inputs and outputs:

 

 - Counter is a Moore type FSM having a state transition diagram in which nodes are arranged in a circle:




- While in general the sequential circuit design method should be used, common cases can be designed in more intuitive manner


COUNTERS - 1

Counters

- Counter inputs and outputs:

 

 - Counter is a Moore type FSM having a state transition diagram in which nodes are arranged in a circle:




- While in general the sequential circuit design method should be used, common cases can be designed in more intuitive manner


COUNTERS - 1

Counters

- Counter inputs and outputs:

 

 - Counter is a Moore type FSM having a state transition diagram in which nodes are arranged in a circle:



- While in general the sequential circuit design method should be used, common cases can be designed in more intuitive manner

COUNTERS - 1

Basic Incrementing Counter

- Consider an n -bit counter that counts from 0 to $2^n - 1$ (and back to 0)
 - ▶ Ex: a 2-bit counter, counts 00, 01, 10, 11, 00, 01,
- Every clock cycle we need to:
 - ▶ Store the current count value
 - ▶ Add 1 to it (increment it) to obtain the next value

COUNTERS - 1

Counter Components



COUNTERS - 1

Counter Components

- How to store n -bits?

COUNTERS - 1


Counter Components

- How to store n -bits? n -bit register

COUNTERS - 1

Counter Components


- How to store n -bits? n -bit register

 

COUNTERS - 1

Counter Components

- How to store n -bits? n -bit register

 


- How to increment an n -bit number?

COUNTERS - 1

Counter Components

- How to store n -bits? n -bit register

 


- How to increment an n -bit number? n -bit incrementer


COUNTERS - 1

Counter Components

- How to store n -bits? n -bit register

 

 - How to increment an n -bit number? n -bit incrementer



COUNTERS - 1

Half Adder

| <i>a</i> | <i>b</i> | <i>s</i> | <i>c</i> |
|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

- SOP formulas:

$$s = \bar{a}b + a\bar{b}$$


$$c = ab$$

- Usually written in terms of XOR function as:

$$s = a \oplus b$$

$$c = ab$$


- Half adder logic circuit:

 

COUNTERS - 1

Incrementing Counter


4-Bit Incrementing Counter

 


COUNTERS - 1

Decrementing Counter

 - An n -bit counter that counts back from $2^n - 1$ to 0 (and back to $2^n - 1$)
 - Ex: a 2-bit counter, counts 11, 10, 01, 00, 11, 10,
- How to store n -bits? n -bit register



 - How to decrement an n -bit number? n -bit decrementer



COUNTERS - 1

Half Subtractor

| x | y | d | b |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

- SOP formulas:

$$d = \bar{x}y + x\bar{y}$$


$$b = \bar{x}y$$

- Usually written in terms of XOR function as:

$$d = x \oplus y$$

$$b = \bar{x}y$$


- Half subtractor logic circuit:

 

COUNTERS - 1

4-Bit Decrementing Counter

4-Bit Decrementing Counter

 

COUNTERS - 1

Applications


- Iteration (“loops”) in logic design
 - ▶ $n \times n$ -bit shift-add multiplier requires n iterations
- Interrupt timers
 - ▶ OS scheduler preempts process after a fixed timeslice
- Software timeouts
 - ▶ Show error if webpage does not load in specified time interval

COUNTERS - 1

Think About It

Incrementer/Decrementer Counter

 - Design an incrementer/decrementer counter




COUNTERS - 1

Think About It

Incrementer/Decrementer Counter

 - Design an incrementer/decrementer counter



- Make the logic as simple as possible