



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Wallace Tree Multiplier - 2

Reetinder Sidhu

Department of Computer Science and Engineering

DIGITAL DESIGN AND COMPUTER ORGANIZATION

Wallace Tree Multiplier - 2

Reetinder Sidhu

Department of Computer Science and
Engineering

WALLACE TREE MULTIPLIER - 2

Course Outline



- Digital Design
 - ▶ Combinational logic design
 - ▶ Sequential logic design
 - ★ **Wallace Tree Multiplier - 2**
- Computer Organization
 - ▶ Architecture (microprocessor instruction set)
 - ▶ Microarchitecture (microprocessor operation)


Concepts covered

- **Wallace Tree Multiplication**

WALLACE TREE MULTIPLIER - 2

Carry Save Adder


Basic Carry Save Adder

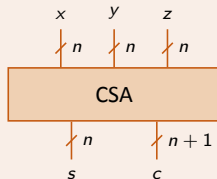

- Contains n full adders
- **Inputs** Three n -bit numbers
- **Outputs**
 - ▶ One n -bit number
 - ▶ One $(n + 1)$ -bit number (whose LSB is 0)


WALLACE TREE MULTIPLIER - 2

Different Sized Inputs to CSA

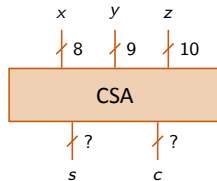

WALLACE TREE MULTIPLIER - 2


Different Sized Inputs to CSA

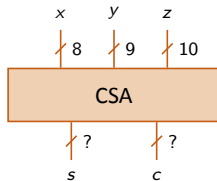

- Sum output size will be same as size of largest input

WALLACE TREE MULTIPLIER - 2


Different Sized Inputs to CSA

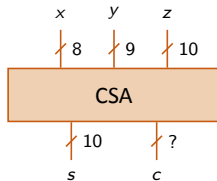

- Sum output size will be same as size of largest input

WALLACE TREE MULTIPLIER - 2


Different Sized Inputs to CSA

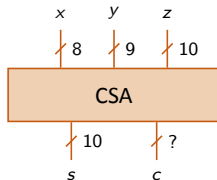

- Sum output size will be same as size of largest input
- Computed carry size will be only 9 bits

WALLACE TREE MULTIPLIER - 2


Different Sized Inputs to CSA

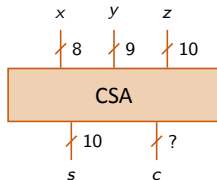

- Sum output size will be same as size of largest input
- Computed carry size will be only 9 bits
- So after left shift carry output is 10 bits

WALLACE TREE MULTIPLIER - 2

Different Sized Inputs to CSA

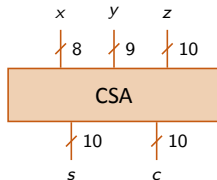

- Sum output size will be same as size of largest input
- Computed carry size will be only 9 bits
- So after left shift carry output is 10 bits


WALLACE TREE MULTIPLIER - 2

- Consider the multiplication of two 8-bit numbers



WALLACE TREE MULTIPLIER - 2

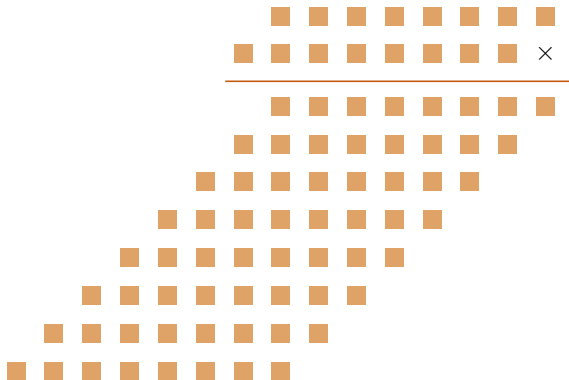- Consider the multiplication of two 8-bit numbers




- 8×8 array of values computed by 8×8 array of two input AND gates

WALLACE TREE MULTIPLIER - 2



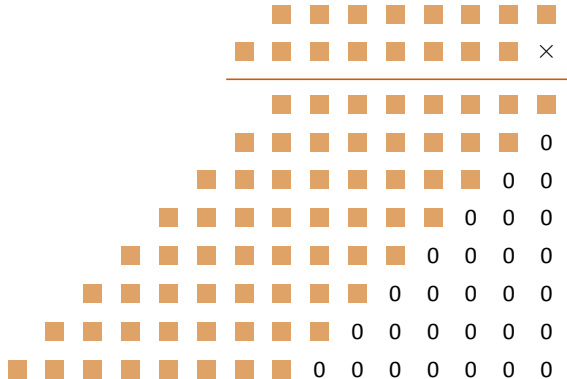
- Consider the multiplication of two 8-bit numbers



- 8 × 8 array of values computed by 8 × 8 array of two input AND gates

WALLACE TREE MULTIPLIER - 2

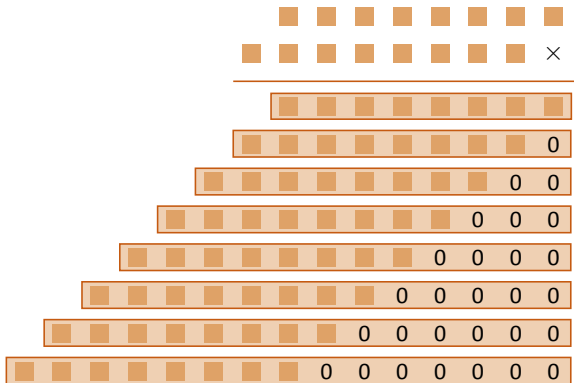
- Consider the multiplication of two 8-bit numbers



- 8×8 array of values computed by 8×8 array of two input AND gates

WALLACE TREE MULTIPLIER - 2

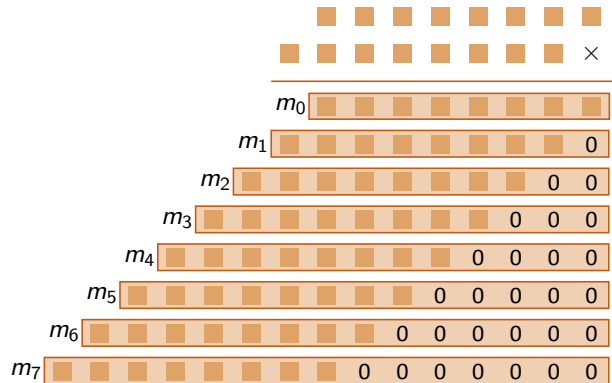
- Consider the multiplication of two 8-bit numbers



- 8×8 array of values computed by 8×8 array of two input AND gates

WALLACE TREE MULTIPLIER - 2

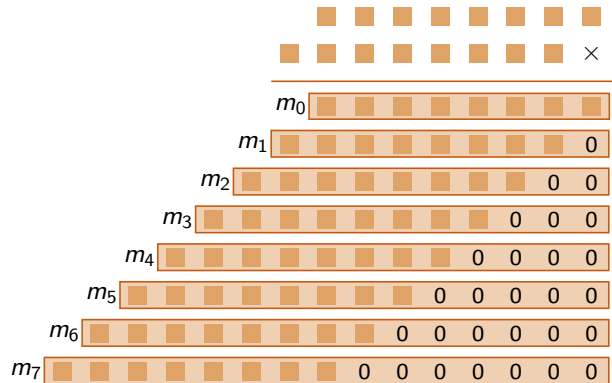
- Consider the multiplication of two 8-bit numbers



- 8×8 array of values computed by 8×8 array of two input AND gates
- m_0, \dots, m_7 are partial products

WALLACE TREE MULTIPLIER - 2

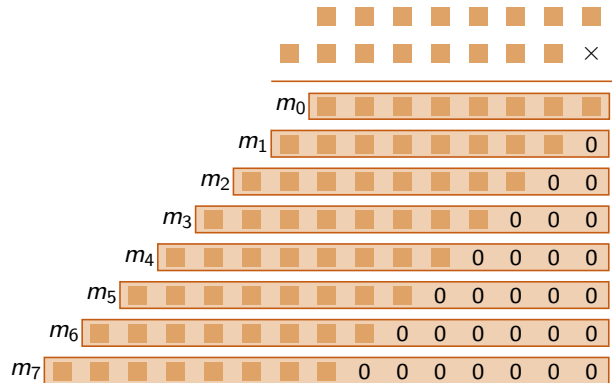
- Consider the multiplication of two 8-bit numbers



- 8×8 array of values computed by 8×8 array of two input AND gates
- m_0, \dots, m_7 are partial products
- m_i has size $8 + i$ bits

WALLACE TREE MULTIPLIER - 2

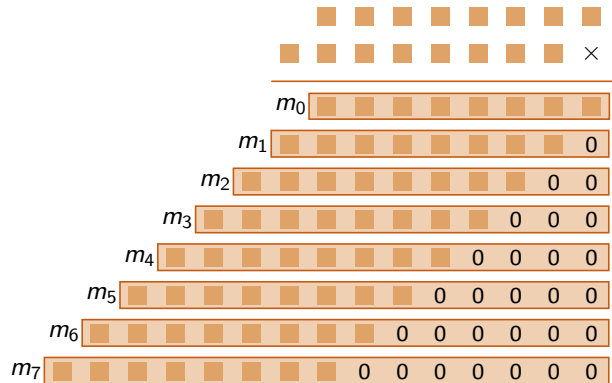- Consider the multiplication of two 8-bit numbers



- 8×8 array of values computed by 8×8 array of two input AND gates
- m_0, \dots, m_7 are partial products
- m_i has size $8 + i$ bits

The problem of multiplying two 8-bit numbers has been reduced to the problem of adding the partial products m_0, \dots, m_7


WALLACE TREE MULTIPLIER - 2

Carry Save Adders




WALLACE TREE MULTIPLIER - 2

Carry Save Adders

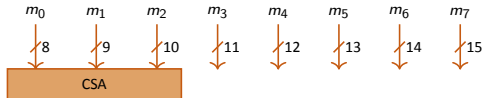


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

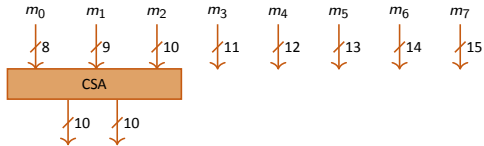


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

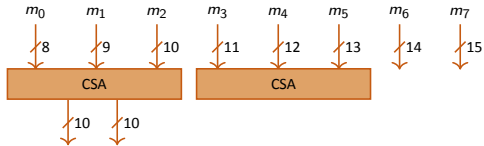


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

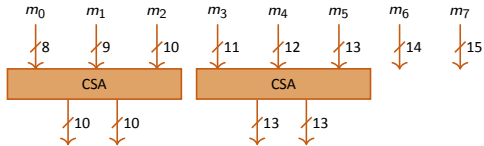


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

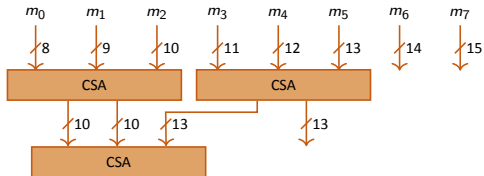


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

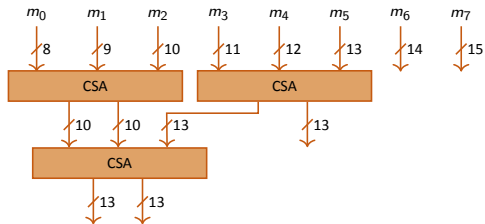


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

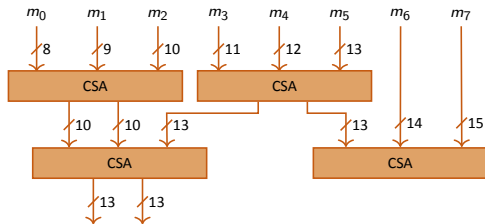


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

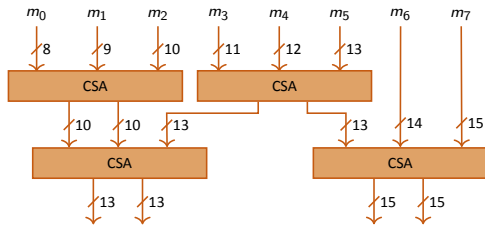


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

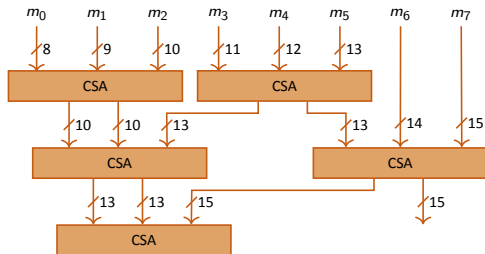


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

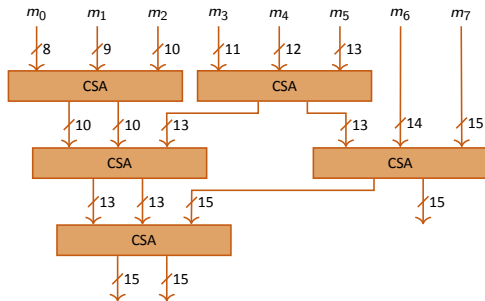


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

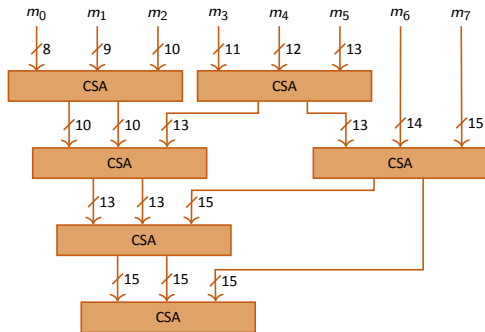


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

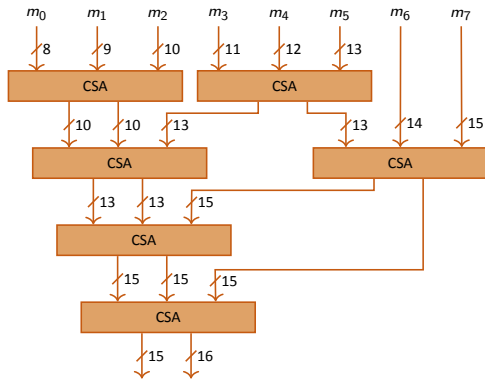


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

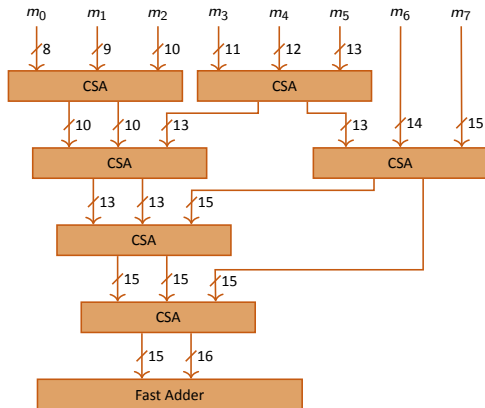


WALLACE TREE MULTIPLIER - 2

Carry Save Adders

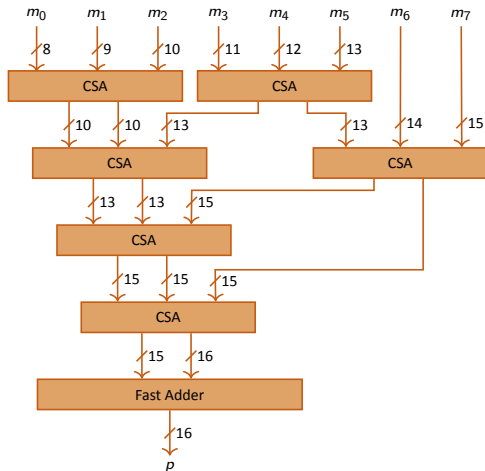

WALLACE TREE MULTIPLIER - 2


Carry Save Adders

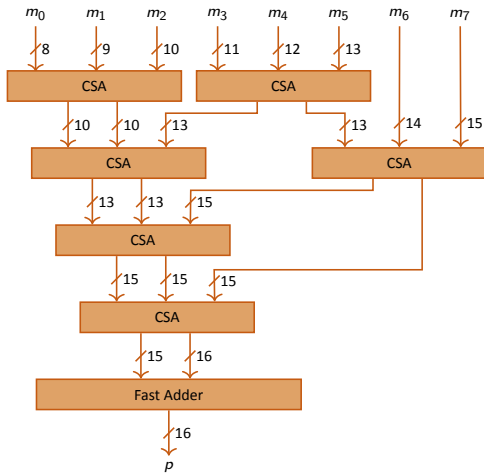

- Let t_{Adder} be critical path delay of fast adder

WALLACE TREE MULTIPLIER - 2


Carry Save Adders

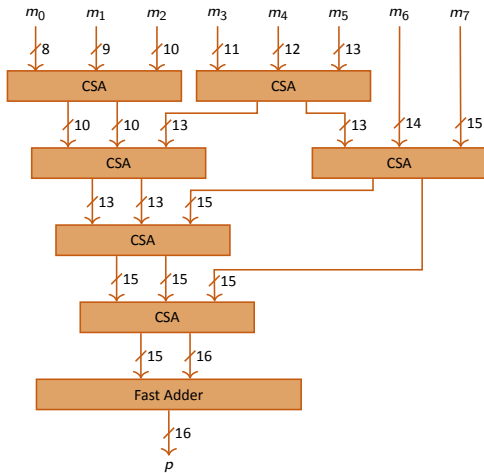

- Let t_{Adder} be critical path delay of fast adder
- The critical path delay of the Wallace tree above the adder is just $4t_{FA}$

WALLACE TREE MULTIPLIER - 2

Carry Save Adders

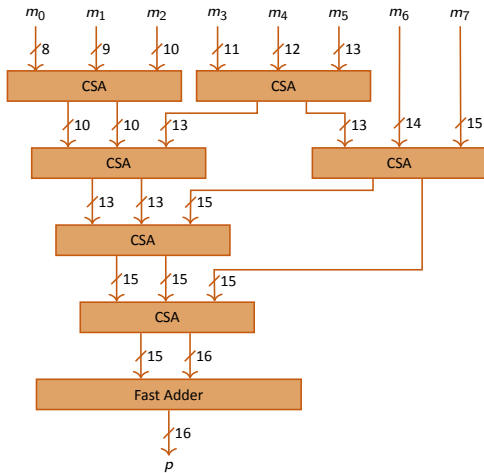

- Let t_{Adder} be critical path delay of fast adder
- The critical path delay of the Wallace tree above the adder is just $4t_{FA}$
- Critical path delay of 8×8 Wallace tree multiplier is thus $t_{AND} + 4t_{FA} + t_{Adder}$

WALLACE TREE MULTIPLIER - 2

Think About It



- Compare the area and time performance of the Wallace Tree Multiplier with that of the Shift-Add Multiplier
 - ▶ Try ripple carry and parallel prefix adders in both