



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Finite State Machines - 2

Reetinder Sidhu

Department of Computer Science and Engineering

DIGITAL DESIGN AND COMPUTER ORGANIZATION

Finite State Machines - 2

Reetinder Sidhu

Department of Computer Science and
Engineering

- Digital Design
 - ▶ Combinational logic design
 - ▶ Sequential logic design
 - ★ **Finite State Machines - 2**
- Computer Organization
 - ▶ Architecture (microprocessor instruction set)
 - ▶ Microarchitecture (microprocessor operation)

Concepts covered

- Finite State Machine Design Example

FINITE STATE MACHINES - 2

How to Design Synchronous Sequential Logic Circuits? (Moore FSM)

- Determine inputs and outputs
- State transition diagram
- Encoding tables
 - ▶ State
 - ▶ Output
- State transition table
- Output table
- Logic minimization
 - ▶ State transition table yields Boolean formulas for next state logic
 - ▶ Output table yields Boolean formulas for output logic
- Logic circuit construction

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic



Source: *platformliftco*

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first



Source: *platformliftco*

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up



Source: *platformliftco*

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up



Source: *platformliftco*

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The lift system has a sensor which indicates when the lift is stationary at one of the floors or is moving between them



Source: platformliftco

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The lift system has a sensor which indicates when the lift is stationary at one of the floors or is moving between them
 - ▶ The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors



Source: *platformliftco*

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The lift system has a sensor which indicates when the lift is stationary at one of the floors or is moving between them
 - ▶ The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors
- Control logic should output signals to control the motor that takes the lift up and down




Source: platformliftco

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

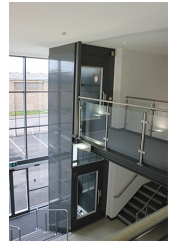- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The lift system has a sensor which indicates when the lift is stationary at one of the floors or is moving between them
 - ▶ The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors
- Control logic should output signals to control the motor that takes the lift up and down
 - ▶ Signal *lift_up* is 1 when the lift should move up and 0 otherwise
 - ▶ Signal *lift_down* is 1 when the lift should move down and 0 otherwise



Source: platformliftco

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The lift system has a sensor which indicates when the lift is stationary at one of the floors or is moving between them
 - ▶ The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors
- Control logic should output signals to control the motor that takes the lift up and down
 - ▶ Signal *lift_up* is 1 when the lift should move up and 0 otherwise
 - ▶ Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- Control logic should also output signals indicating which floor the lift is on



Source: *platformliftco*

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The lift system has a sensor which indicates when the lift is stationary at one of the floors or is moving between them
 - ▶ The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors
- Control logic should output signals to control the motor that takes the lift up and down
 - ▶ Signal *lift_up* is 1 when the lift should move up and 0 otherwise
 - ▶ Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- Control logic should also output signals indicating which floor the lift is on
 - ▶ *on_ground* is 1 when the lift is on ground floor and 0 otherwise
 - ▶ *on_first* is 1 when lift is on first floor and 0 otherwise




Source: platformliftco

FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

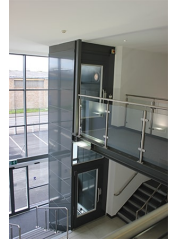- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The lift system has a sensor which indicates when the lift is stationary at one of the floors or is moving between them
 - ▶ The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors
- Control logic should output signals to control the motor that takes the lift up and down
 - ▶ Signal *lift_up* is 1 when the lift should move up and 0 otherwise
 - ▶ Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- Control logic should also output signals indicating which floor the lift is on
 - ▶ *on_ground* is 1 when the lift is on ground floor and 0 otherwise
 - ▶ *on_first* is 1 when lift is on first floor and 0 otherwise
- Elevator initially on ground floor



Source: platformliftco


FINITE STATE MACHINES - 2

Lift (Elevator) Control Logic

- Problem is to design the control logic for a lift in a building of two floors: ground and first
- The lift has a switch with two positions, down and up, which respectively indicate that the lift should go down or up
 - ▶ The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The lift system has a sensor which indicates when the lift is stationary at one of the floors or is moving between them
 - ▶ The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors
- Control logic should output signals to control the motor that takes the lift up and down
 - ▶ Signal *lift_up* is 1 when the lift should move up and 0 otherwise
 - ▶ Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- Control logic should also output signals indicating which floor the lift is on
 - ▶ *on_ground* is 1 when the lift is on ground floor and 0 otherwise
 - ▶ *on_first* is 1 when lift is on first floor and 0 otherwise
- Elevator initially on ground floor



Source: platformliftco

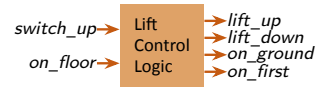

FINITE STATE MACHINES - 2

State Transition Diagram



State Transition Diagram

- A visual representation of an FSM
 - ▶ States represent by circles (called **nodes/vertices**)
 - ▶ Transitions between states represented by directed line segments (called **arcs/edges/arrows**)
 - ▶ Each edge is labeled with a Boolean formula of inputs corresponding to the transition
- In each clock cycle, only one state is **active**
- Active state transitions occur at the rising edge of the clock signal
- If a state is active in the current clock cycle, and it has an outgoing transition labeled with a Boolean formula which is 1 in that clock cycle, then the destination state of the transition will be the active state in the next clock cycle

FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

Elevator Example State Transition Diagram

FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

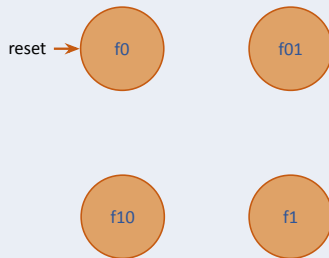Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

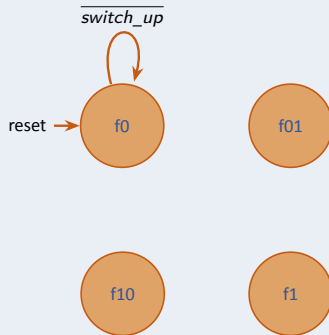Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

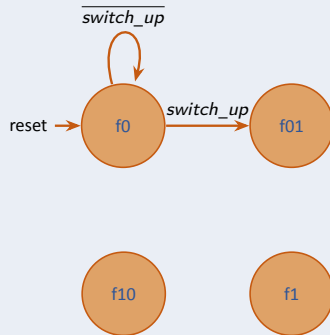Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

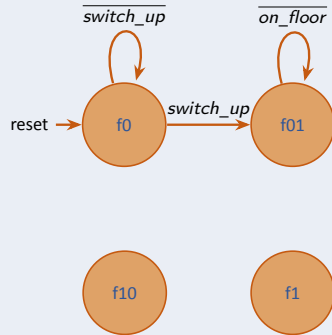Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

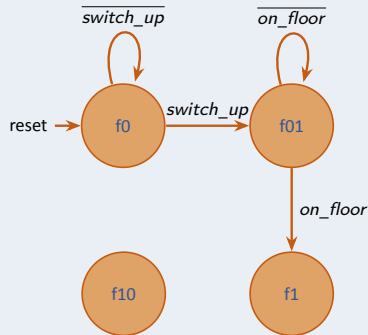Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

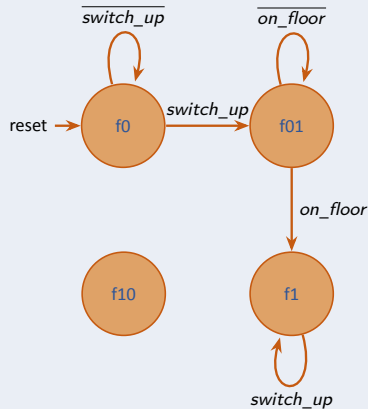Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

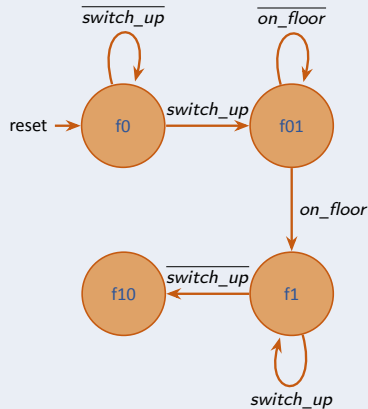Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- The switch signal *switch_up* is 0 when the switch indicates the lift should go down and 1 when switch indicates it should go up
- The sensor signal *on_floor* is 1 when the lift is at ground or first floor, and 0 when the lift is moving between floors

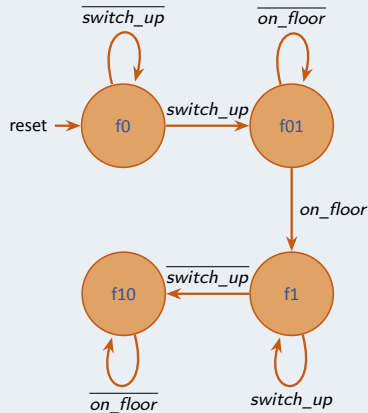
Elevator Example State Transition Diagram



FINITE STATE MACHINES - 2

State Transition Diagram

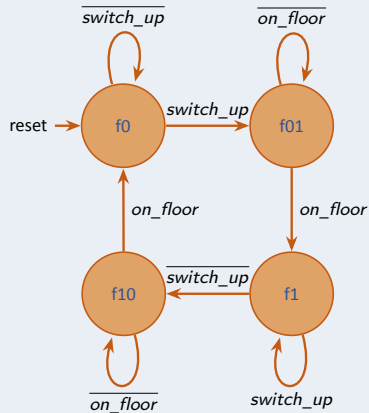Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

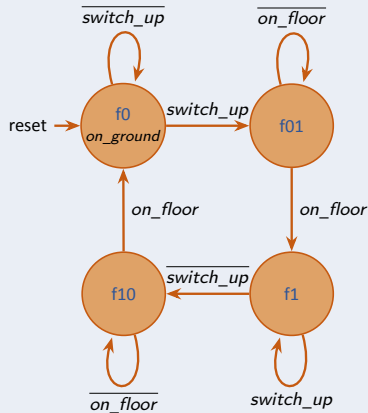Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

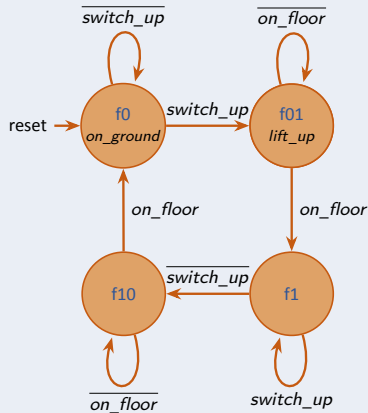Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

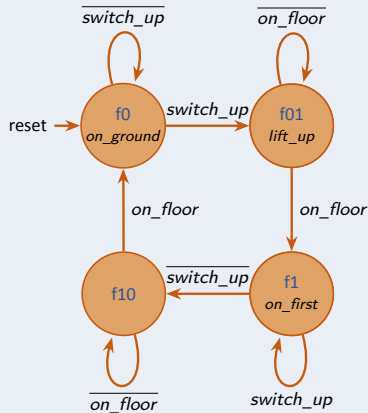Elevator Example State Transition Diagram




FINITE STATE MACHINES - 2

State Transition Diagram

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

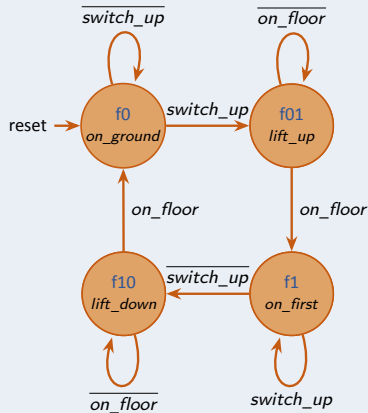Elevator Example State Transition Diagram



FINITE STATE MACHINES - 2

State and Output Encoding Tables

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

FINITE STATE MACHINES - 2

State and Output Encoding Tables

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

Elevator State Encoding Table

State	Encoding ($s_1 s_0$)
f0	00
f01	01
f1	11
f10	10

FINITE STATE MACHINES - 2

State and Output Encoding Tables

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

Elevator State Encoding Table

State	Encoding ($s_1 s_0$)
f0	00
f01	01
f1	11
f10	10

Elevator Output Encoding Tables

FINITE STATE MACHINES - 2

State and Output Encoding Tables

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

Elevator State Encoding Table

State	Encoding ($s_1 s_0$)
f0	00
f01	01
f1	11
f10	10

Elevator Output Encoding Tables

- *on_ground*

Meaning	Encoding
Lift on ground floor	1
Lift anywhere else	0

FINITE STATE MACHINES - 2

State and Output Encoding Tables

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

Elevator State Encoding Table

State	Encoding ($s_1 s_0$)
f0	00
f01	01
f1	11
f10	10

Elevator Output Encoding Tables

- *on_ground*

Meaning	Encoding
Lift on ground floor	1
Lift anywhere else	0

- *on_first*

Meaning	Encoding
Lift on first floor	1
Lift anywhere else	0

FINITE STATE MACHINES - 2

State and Output Encoding Tables

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

Elevator State Encoding Table

State	Encoding ($s_1 s_0$)
f0	00
f01	01
f1	11
f10	10

Elevator Output Encoding Tables

- *on_ground*

Meaning	Encoding
Lift on ground floor	1
Lift anywhere else	0

- *on_first*

Meaning	Encoding
Lift on first floor	1
Lift anywhere else	0

- *lift_up*

Meaning	Encoding
Lift going from ground to first floor	1
Lift anywhere else	0

FINITE STATE MACHINES - 2

State and Output Encoding Tables

- Signal *lift_up* is 1 when the lift should move up and 0 otherwise
- Signal *lift_down* is 1 when the lift should move down and 0 otherwise
- *on_ground* is 1 when the lift is on ground floor and 0 otherwise
- *on_first* is 1 when lift is on first floor and 0 otherwise

Elevator State Encoding Table

State	Encoding ($s_1 s_0$)
f0	00
f01	01
f1	11
f10	10

Elevator Output Encoding Tables

- *on_ground*

Meaning	Encoding
Lift on ground floor	1
Lift anywhere else	0

- *on_first*

Meaning	Encoding
Lift on first floor	1
Lift anywhere else	0

- *lift_up*


Meaning	Encoding
Lift going from ground to first floor	1
Lift anywhere else	0

- *lift_down*

Meaning	Encoding
Lift going from first to ground floor	1
Lift anywhere else	0

FINITE STATE MACHINES - 2

State Transition Table

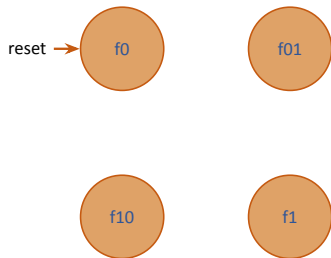


Elevator Example State Transition Table

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

FINITE STATE MACHINES - 2

State Transition Table

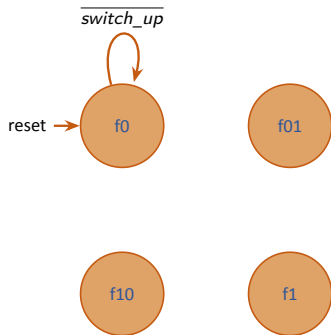


Elevator Example State Transition Table

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

FINITE STATE MACHINES - 2

State Transition Table

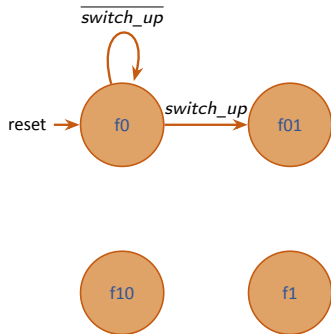


Elevator Example State Tansition Table

Current State		Inputs		Next Sate	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

FINITE STATE MACHINES - 2

State Transition Table

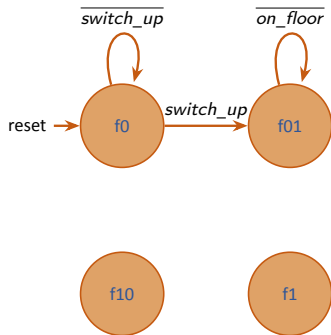


Elevator Example State Transition Table

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1		
0	1	1	0	0	1
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

FINITE STATE MACHINES - 2

State Transition Table

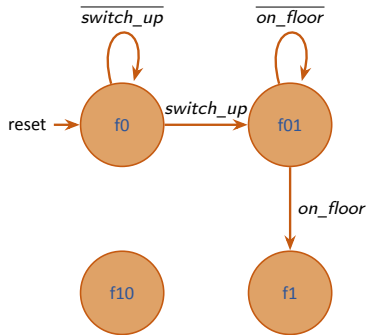


Elevator Example State Tansition Table

Current State		Inputs		Next Sate	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

FINITE STATE MACHINES - 2

State Transition Table

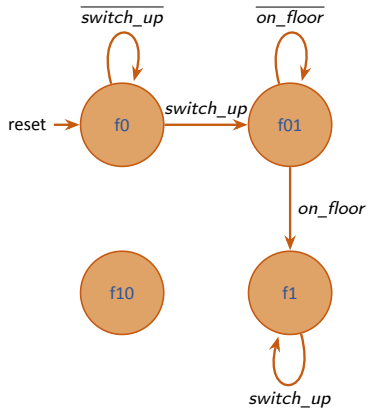


Elevator Example State Tansition Table

Current State		Inputs		Next Sate	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0	1	1
1	1	1	1	1	1

FINITE STATE MACHINES - 2

State Transition Table

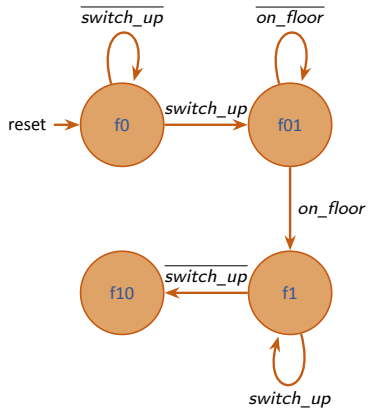


Elevator Example State Tansition Table

Current State		Inputs		Next Sate	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

FINITE STATE MACHINES - 2

State Transition Table

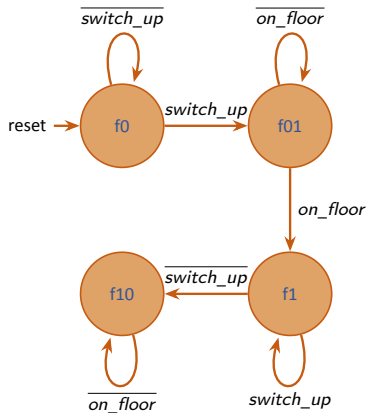


Elevator Example State Tansition Table

Current State		Inputs		Next Sate	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1		
1	0	1	0	1	0
1	0	1	1		
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

FINITE STATE MACHINES - 2

State Transition Table

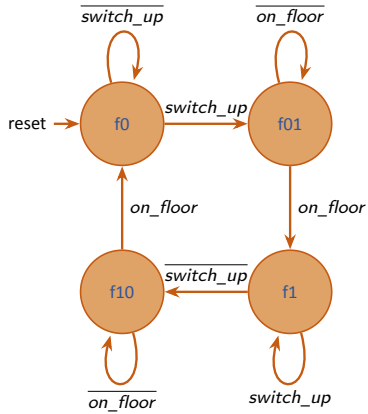


Elevator Example State Transition Table

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

FINITE STATE MACHINES - 2

Output Table

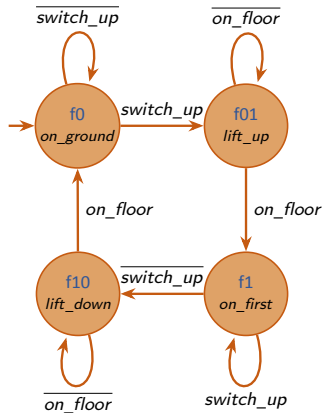


Elevator Example Output Table

State		Outputs			
s_1	s_0	<i>on_ground</i>	<i>on_first</i>	<i>lift_up</i>	<i>lift_down</i>
0	0				
0	1				
1	0				
1	1				

FINITE STATE MACHINES - 2

Output Table

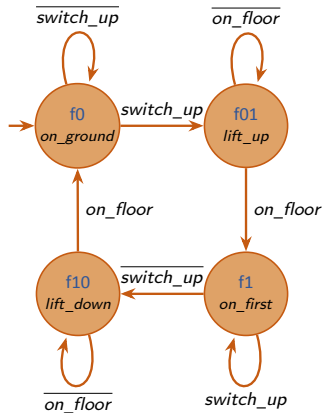


Elevator Example Output Table

State		Outputs			
s_1	s_0	<i>on_ground</i>	<i>on_first</i>	<i>lift_up</i>	<i>lift_down</i>
0	0	1			
0	1				
1	0				
1	1				

FINITE STATE MACHINES - 2

Output Table

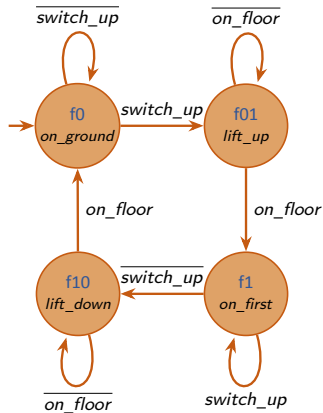


Elevator Example Output Table

State		Outputs			
s_1	s_0	on_ground	on_first	$lift_up$	$lift_down$
0	0	1			
0	1	0			
1	0	0			
1	1	0			

FINITE STATE MACHINES - 2

Output Table

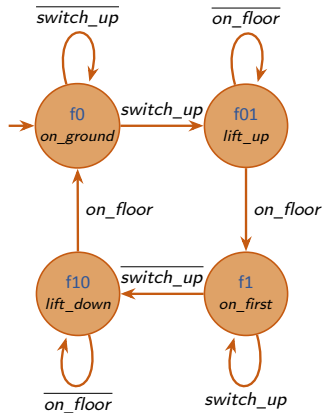


Elevator Example Output Table

State		Outputs			
s_1	s_0	<i>on_ground</i>	<i>on_first</i>	<i>lift_up</i>	<i>lift_down</i>
0	0	1			
0	1	0		1	
1	0	0			
1	1	0			

FINITE STATE MACHINES - 2

Output Table

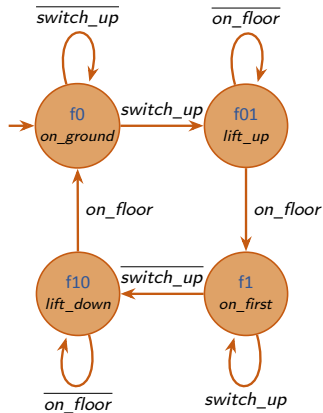


Elevator Example Output Table

State		Outputs			
s_1	s_0	<i>on_ground</i>	<i>on_first</i>	<i>lift_up</i>	<i>lift_down</i>
0	0	1		0	
0	1	0		1	
1	0	0		0	
1	1	0		0	

FINITE STATE MACHINES - 2

Output Table

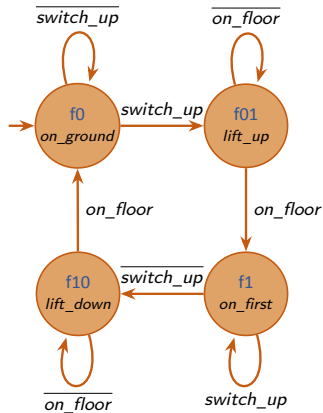


Elevator Example Output Table

State		Outputs			
s_1	s_0	<i>on_ground</i>	<i>on_first</i>	<i>lift_up</i>	<i>lift_down</i>
0	0	1		0	
0	1	0		1	
1	0	0		0	
1	1	0	1	0	

FINITE STATE MACHINES - 2

Output Table

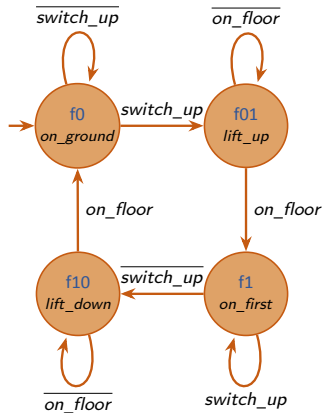


Elevator Example Output Table

State		Outputs			
s_1	s_0	on_ground	on_first	$lift_up$	$lift_down$
0	0	1	0	0	
0	1	0	0	1	
1	0	0	0	0	
1	1	0	1	0	

FINITE STATE MACHINES - 2

Output Table

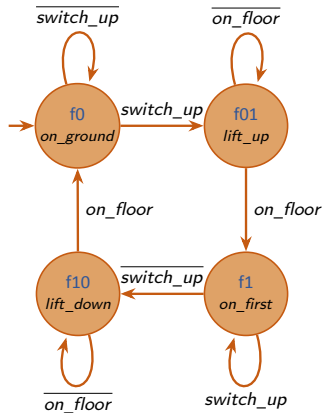


Elevator Example Output Table

State		Outputs			
s_1	s_0	on_ground	on_first	$lift_up$	$lift_down$
0	0	1	0	0	
0	1	0	0	1	
1	0	0	0	0	1
1	1	0	1	0	

FINITE STATE MACHINES - 2

Output Table

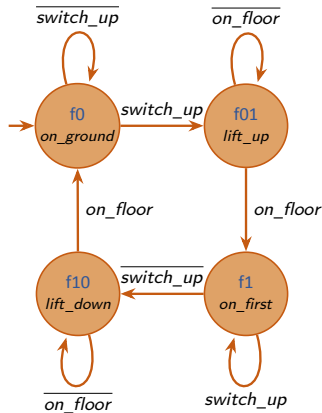

Elevator Example Output Table

State		Outputs			
s_1	s_0	on_ground	on_first	$lift_up$	$lift_down$
0	0	1	0	0	0
0	1	0	0	1	0
1	0	0	0	0	1
1	1	0	1	0	0

FINITE STATE MACHINES - 2

Logic Minimization (State)

FINITE STATE MACHINES - 2

Logic Minimization (State)

- State transition table:

Current State		Inputs		Next State	
s_1	s_0	<i>switch_up</i>	<i>on_floor</i>	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

FINITE STATE MACHINES - 2

Logic Minimization (State)

- State transition table:

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

Minimized Boolean Formula

- K-map for s'_1 :

		$switch_up \quad on_floor$			
		00	01	11	10
$s_1 s_0$	00				
	01				
	11				
	10				

FINITE STATE MACHINES - 2

Logic Minimization (State)

- State transition table:

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

Minimized Boolean Formula

- K-map for s'_1 :

		$switch_up \quad on_floor$			
		00	01	11	10
$s_1 s_0$	00	0	0	0	0
	01	0	1	1	0
	11	1	1	1	1
	10	1	0	0	1

FINITE STATE MACHINES - 2

Logic Minimization (State)

- State transition table:

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

Minimized Boolean Formula

- K-map for s'_1 :

		$switch_up \quad on_floor$			
		00	01	11	10
$s_1 s_0$	00	0	0	0	0
	01	0	1	1	0
	11	1	1	1	1
	10	1	0	0	1

- Minimized formula:

$$s'_1 = s_1 s_0 + s_1 on_floor + s_0 on_floor$$

FINITE STATE MACHINES - 2

Logic Minimization (State)

- State transition table:

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

Minimized Boolean Formula

- K-map for s'_0 :

		cd			
		00	01	11	10
ab	00				
	01				
	11				
	10				

FINITE STATE MACHINES - 2

Logic Minimization (State)

- State transition table:

Current State		Inputs		Next State	
s_1	s_0	<i>switch_up</i>	<i>on_floor</i>	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

Minimized Boolean Formula

- K-map for s'_0 :

		cd			
		00	01	11	10
ab	00	0	0	1	1
	01	1	1	1	1
	11	0	0	1	1
	10	0	0	0	0

FINITE STATE MACHINES - 2

Logic Minimization (State)

- State transition table:

Current State		Inputs		Next State	
s_1	s_0	$switch_up$	on_floor	s'_1	s'_0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	1

Minimized Boolean Formula

- K-map for s'_0 :

		cd			
		00	01	11	10
ab	00	0	0	1	1
	01	1	1	1	1
	11	0	0	1	1
	10	0	0	0	0

- Minimized formula:

$$s'_0 = \overline{s_1} s_0 + \overline{s_1} switch_up + s_0 switch_up$$

FINITE STATE MACHINES - 2

Logic Diagram

- Next state formulas:

- ▶ $s'_1 = s_1 s_0 + s_1 \overline{on_floor} + s_0 on_floor$
- ▶ $s'_0 = \overline{s_1} s_0 + \overline{s_1} switch_up + s_0 switch_up$

- Output formulas:

- ▶ $on_ground = \overline{s_1} \overline{s_0}$
- ▶ $on_first = s_1 s_0$
- ▶ $lift_up = \overline{s_1} s_0$
- ▶ $lift_down = s_1 \overline{s_0}$

FINITE STATE MACHINES - 2

Logic Diagram


- Next state formulas:

- ▶ $s_1' = s_1 s_0 + s_1 \overline{\text{on_floor}} + s_0 \text{on_floor}$
- ▶ $s_0' = \overline{s_1} s_0 + \overline{s_1} \text{switch_up} + s_0 \text{switch_up}$

- Output formulas:

- ▶ $\text{on_ground} = \overline{s_1} \overline{s_0}$
- ▶ $\text{on_first} = s_1 s_0$
- ▶ $\text{lift_up} = \overline{s_1} s_0$
- ▶ $\text{lift_down} = s_1 \overline{s_0}$

Elevator Example Logic Diagram

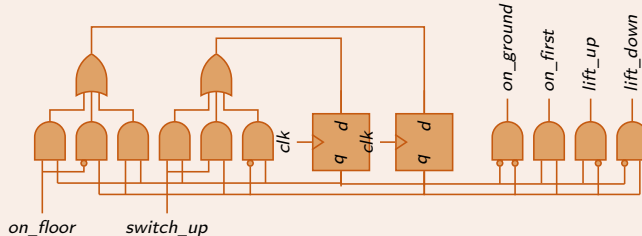

FINITE STATE MACHINES - 2

Think About It



Design of a Moore FSM for traffic light controller (section 3.4.1 of your textbook)