



END SEMESTER ASSESSMENT (ESA) B. Tech II SEMESTER- May '19
UE18EC101 - BASIC ELECTRONICS (Common to all branches)

Time: 3 Hrs

Answer All The Questions

Max Marks: 100

1.	a.	Count the number of branches and nodes in the circuit. If $i_x = 3A$ and the 18 V source delivers 8A of current, what is the value of R_A ? Use Ohm's law as well as KCL.	6
	b.	Reverse saturation current of Ge diode is 200uA at 27°C. If temperature is increased by 30°C find I_S and I_D for the bias voltage of 0.2V at new temperature. If it were Silicon diode what is the current at 27°C ideally.	6
	c.	Explain diode models with the help of equivalent circuits and V-I characteristics. Find V_{O1} , and V_{O2} for the circuit shown considering practical diodes. $R_1 = 1.2k\Omega$, $R_2 = 3.3k\Omega$	8
2.	a.	Explain the operation of the circuit shown along with the required equivalent circuits and waveforms. Calculate the output DC level and the required PIV of each diode.	8
	b.	Draw the circuit diagram of a center tapped FWR with capacitor filter. If the filter capacitor is 120 uF and load current is 80mA calculate the % ripple of the output. The FWR is operating from 50Hz supply and develops a peak rectified voltage of 25V.	6
	c.	Design a Zener regulator that maintains V_0 at 10V for input voltage variation of $20V \pm 10\%$ and load current variation of $30mA \pm 20\%$. Given $I_{zmin} = 2mA$ and $I_{zmax} = 50mA$. Draw the circuit indicating the values of all the components.	6
3.	a.	Simplify the Boolean expression $Y = A(B + C(AB + AC)^*)$ showing the steps involved, also implement the simplified expression using 2 input NAND gates.	6
	b.	Write Sum and Carry expression for Full Adder and implement it using 4:1 Multiplexer. Draw the circuit considering C_{in} as Data line and A,B as select lines. Write the data line input to D_0, D_1, D_2, D_3	8

	c.	Starting from LSB load the data 1010 into SISO Shift register. Explain the operation using negative edge triggered D flip flop along with circuit, state table and timing diagrams.	6
4.	a.	Draw and explain the input and output characteristics of transistor in CE configuration. Mark all the regions of operation stating the biasing conditions for these regions.	8
	b.	Draw and explain the structure of the N channel E- MOSFET. Given $I_{D(ON)}=3\text{mA}$ at $V_{GS(ON)}=10\text{V}$ for an enhancement type of MOSFET with $V_T=3\text{V}$. Find K and the drain current for $V_{GS}=8\text{V}$ indicating all the steps involved and formula used.	6
	c.	The input power to a device is 10,000 W at a voltage of 1000 V. The output power is 500 W, while the output impedance is 20Ω . Find the power and voltage gain in decibels.	6
5.	a.	Define and write ideal values along with the units of the following parameters of Operational Amplifier - i) CMRR, ii) GBW, iii) Slew rate.	6
	b.	Name any one open loop application of Op Amp. Explain this application in detail.	6
	c.	Identify the stages and find the output voltage at each stage. $V_{i_1} = 0.25\text{V}$ $V_i = 2\text{V}$ $V_o = 0.5\text{V}$	8

