



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Dr. Reetinder Sidhu

Department of Computer Science and Engineering

DIGITAL DESIGN AND COMPUTER ORGANIZATION

Multi-Cycle Processor - 1




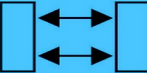
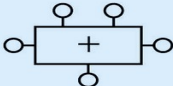

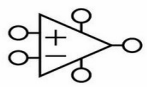

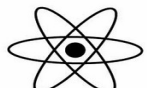
Dr. Reetinder Sidhu

Department of Computer Science and Engineering

Multi-Cycle Processor - 1

Outline

- Introduction
- Performance Analysis
- Multicycle Processor Datapath
- Multicycle Processor Control Logic

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Multi-Cycle Processor - 1


Introduction

- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals

Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

Multi-Cycle Processor - 1

Review: ALU

 


$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT

Multi-Cycle Processor - 1

Architecture State Elements

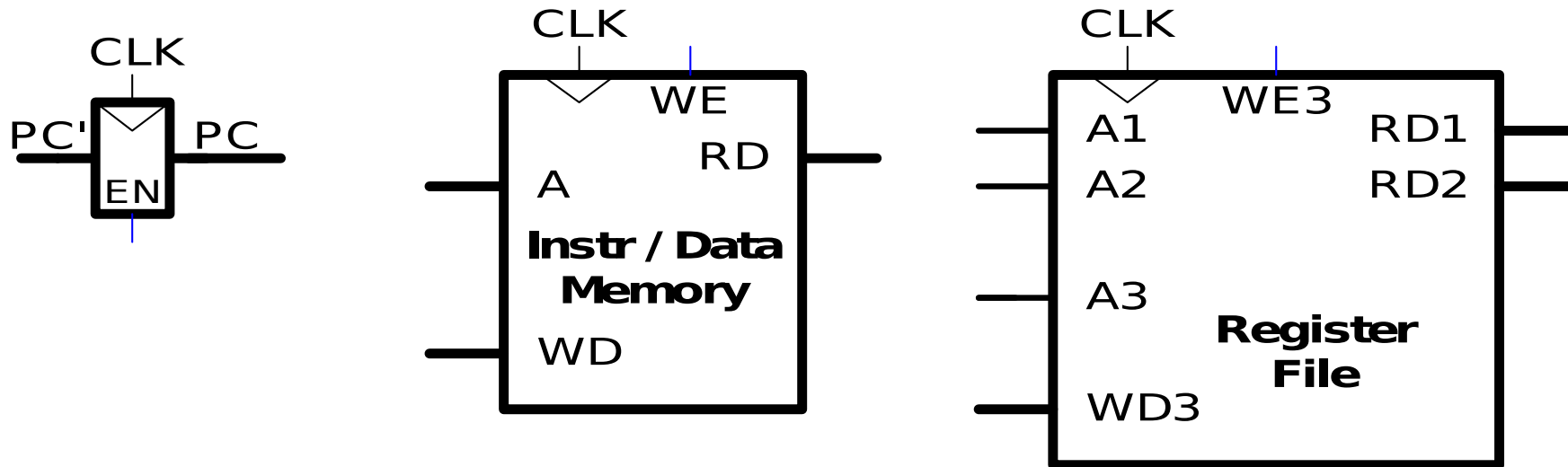- Program Counter, Register File and Main memory
- Latter outside microprocessor



Multi-Cycle Processor - 1

Reading Word-Addressable Memory


- Memory read called *load*
- **Mnemonic:** *load word* (lw)
- **Format:**
lw \$s0, 5(\$t1)
- **Address calculation:**
 - add *base address* (\$t1) to the *offset* (5)
 - address = (\$t1 + 5)
- **Result:**
 - \$s0 holds the value at address (\$t1 + 5)

Any register may be used as base address

Multi-Cycle Processor - 1

Multicycle Datapath: Instruction Fetch


STEP 0: Fetch instruction

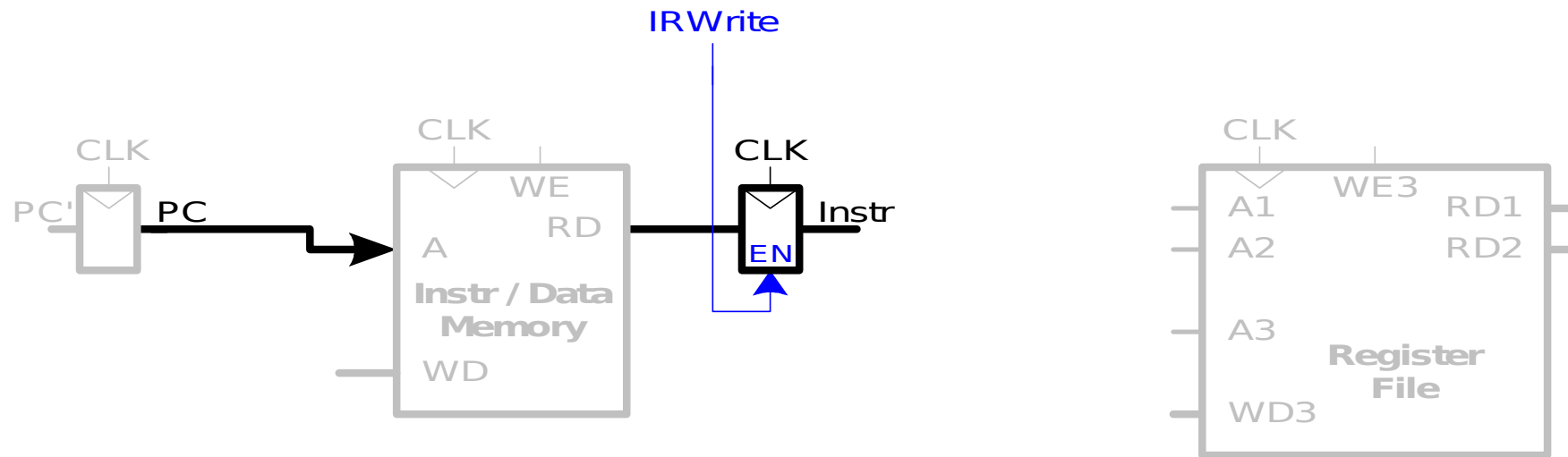

Multi-Cycle Processor - 1

Multicycle Datapath: lw Register Read


STEP 1: Read source operands from RF

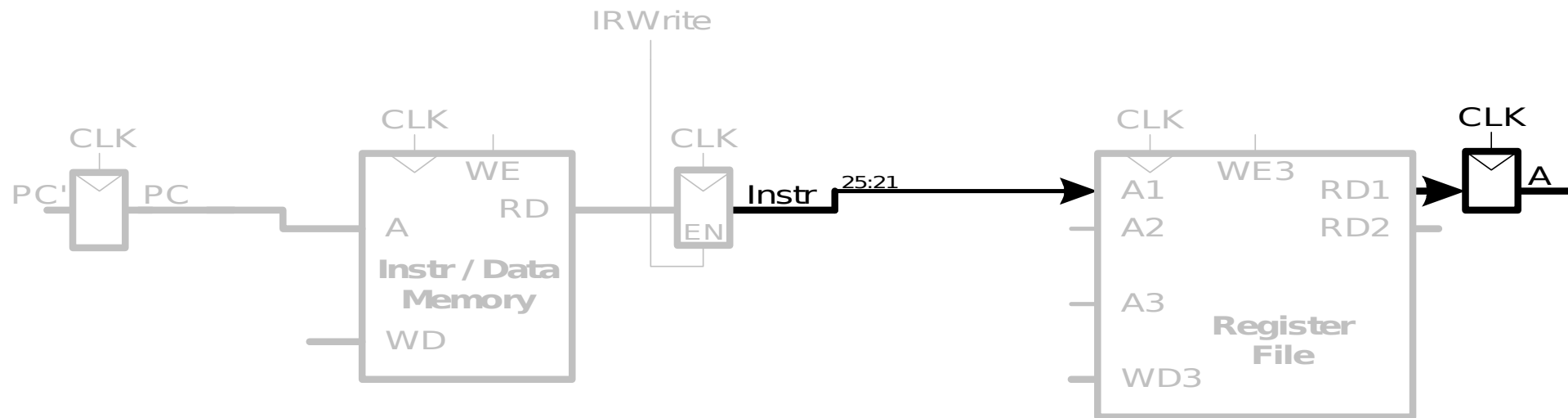

Multi-Cycle Processor - 1

Multicycle Datapath: lw Immediate

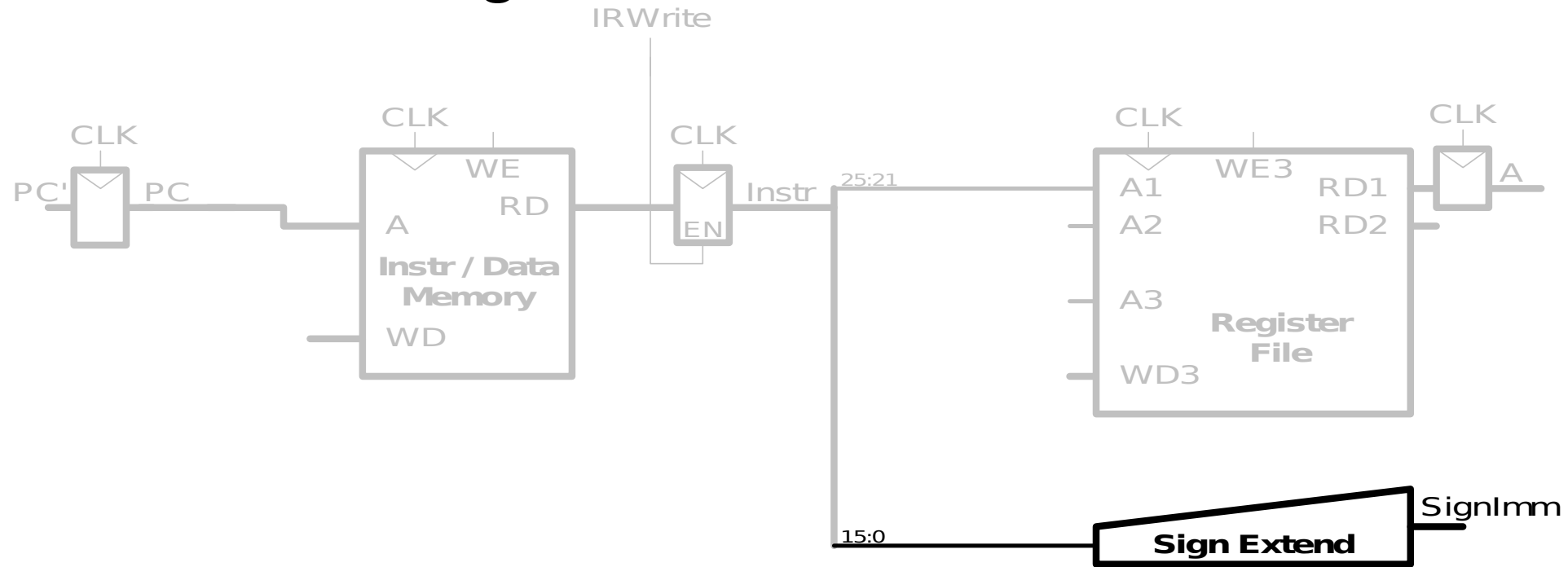
STEP 2: Read and Sign-extend the immediate



Multi-Cycle Processor - 1

Multicycle Datapath: lw Address


STEP 3: Compute the memory address

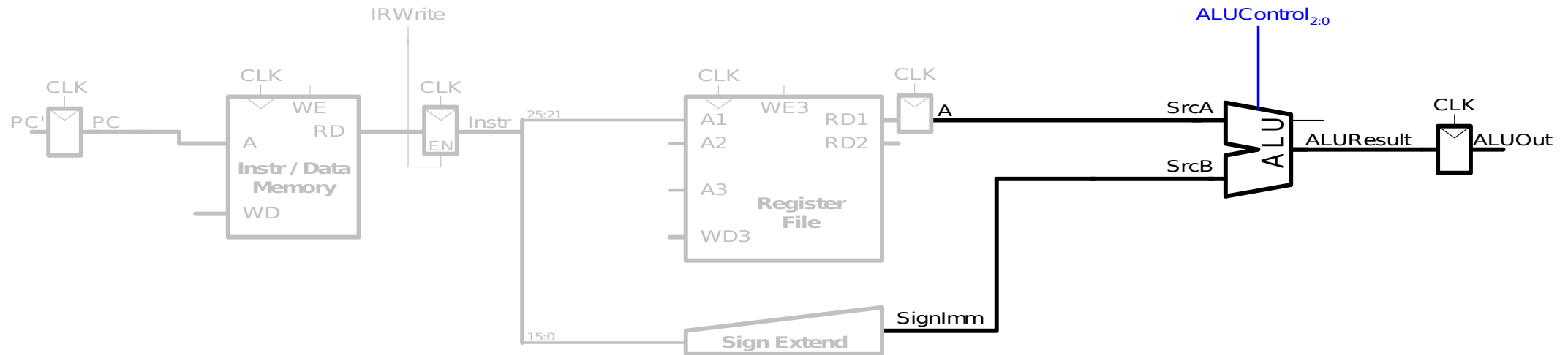

Multi-Cycle Processor - 1

Multicycle Datapath: lw Memory Read


STEP 4: Read data from memory

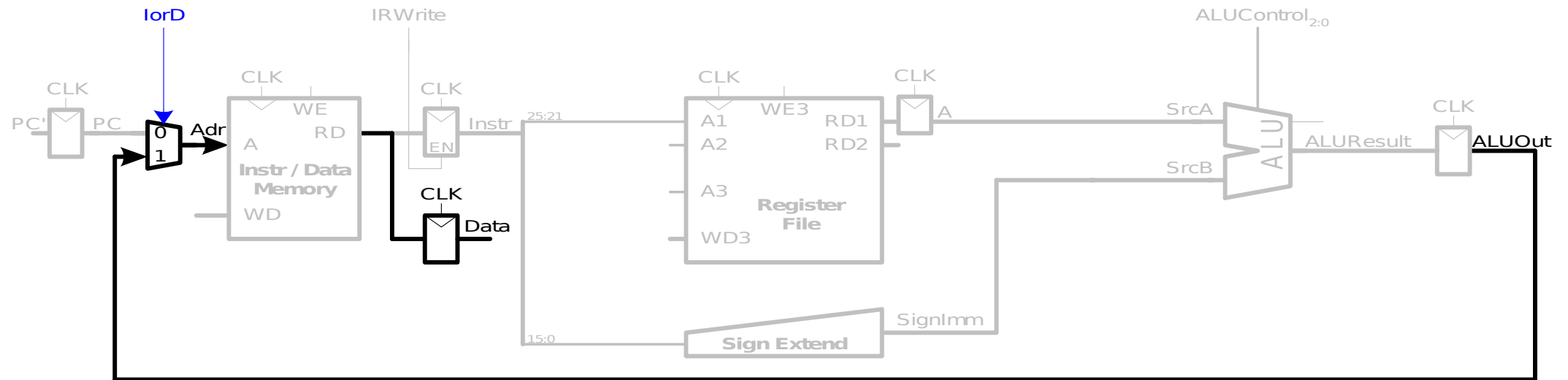


Multi-Cycle Processor - 1

Multicycle Datapath: Lw Write Register

STEP 5: Write data back to register file

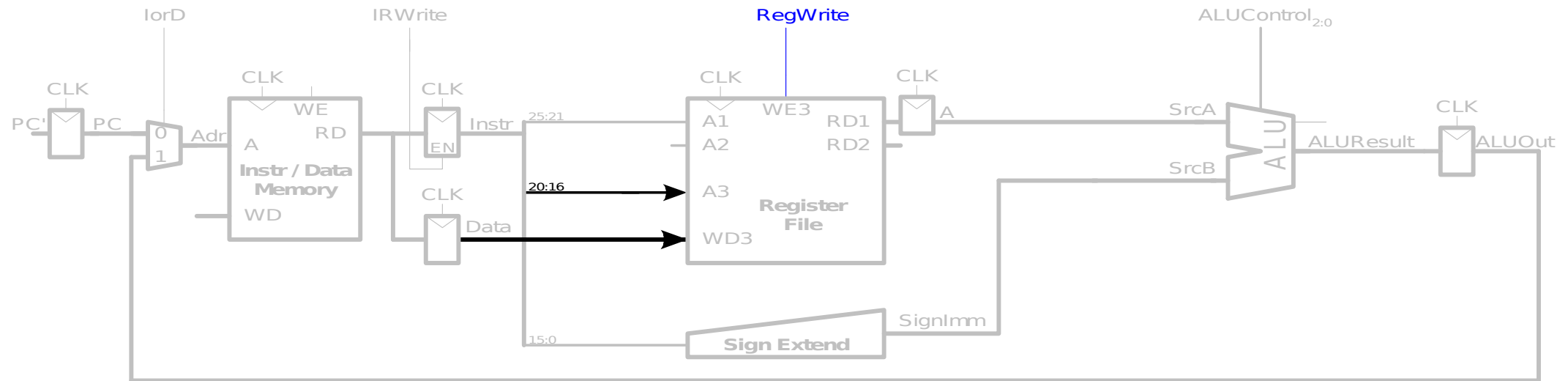

STEP 6: Increment PC

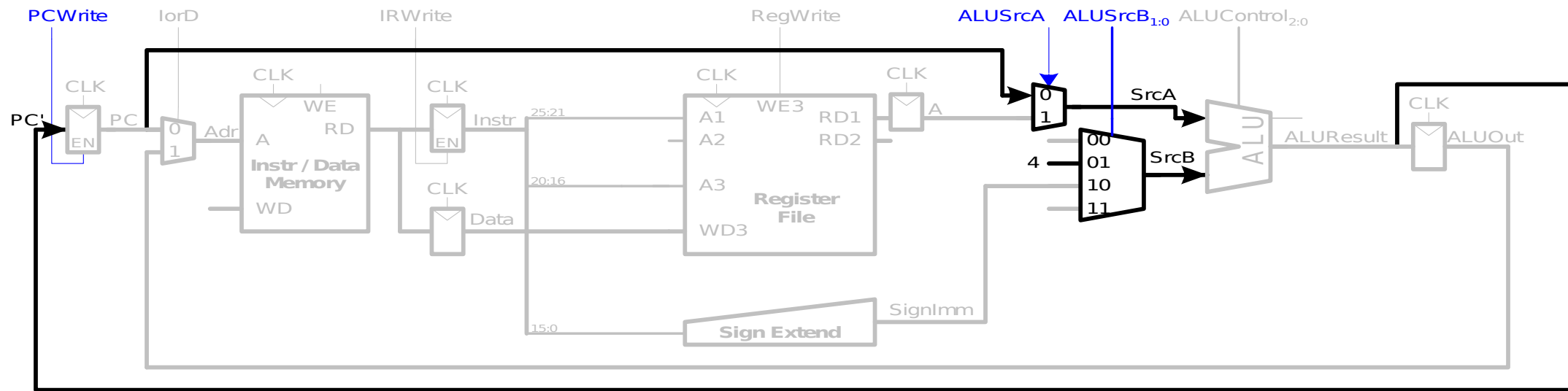

Multi-Cycle Processor

Think About It

- Only one adder (inside ALU)
- In lab datapath design, two adders used (separate adder for PC)
- Would using two adders in current design help? How?
- Note that in both cases, architecture remains the same