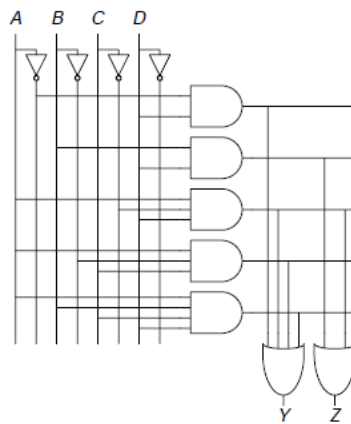


PES University
Department of Computer science and Engineering
Digital Design and Computer Organization
Logic Minimization and K-maps

- Simplify the following Boolean equations using Boolean theorems. Check for correctness using a truth table or K-map.
 a) $Y = AC + A'B'C$ b) $Y = A'B' + A'BC' + (A+C)'$ c)
 $Y = A'B'C'D' + AB'C' + AB'CD' + ABD + A'B'CD' + BC'D + A'$
- Simplify the following Boolean equations using Boolean theorems. Check for correctness using a truth table or K-map.
 (a) $Y = A'BC + A'BC'$
 (b) $Y = A + (A'B + A'B')' + (A+B')$
 (c) $Y = ABC + ABD + ABE + ACD + ACE + (A+D+E)' + B'C'D + B'C'E + B'D'E' + C'D'E'$
- Simplify each of the following Boolean equations. Sketch a reasonably simple combinational circuit implementing the simplified equation.
 (a) $Y = A'BC + (BC')' + BC$
 (b) $Y = (A + B + C)'D + AD + B$
 (c) $Y = ABCD + A'BC'D + (B' + D)'E$
- Write Boolean equations for the circuit in Figure given below. You need not minimize the equations



- Find a minimal Boolean equation for the function in truth table given below. Remember to take advantage of the don't care entries.

Truth Table

A	B	C	D	Y
0	0	0	0	X
0	0	0	1	X
0	0	1	0	X
0	0	1	1	0

0	1	0	0	0
0	1	0	1	X
0	1	1	0	0
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

6. Find a minimal Boolean equation for the function in Figure below. Remember to take advantage of the don't care entries.

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	X
0	0	1	1	X
0	1	0	0	0
0	1	0	1	X
0	1	1	0	X
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

7. Complete the design of the seven-segment decoder segments S_c through S_g .

(a) Derive Boolean equations for the outputs S_c through S_g assuming that inputs greater than 9 must produce blank (0) outputs.

(b) Derive Boolean equations for the outputs S_c through S_g assuming that inputs greater than 9 are don't cares.

(c) Sketch a reasonably simple gate-level implementation of part (b). Multiple outputs can share gates where appropriate.

8. A circuit has four inputs and two outputs. The inputs, $A_3:0$, represent a number from 0 to 15. Output P should be TRUE if the number is prime (0 and 1 are not prime, but 2, 3, 5, and so on, are prime). Output D should be TRUE if the number is divisible by 3. Give simplified Boolean equations for each output and sketch a circuit.

9. Design a circuit that will tell whether a given month has 31 days in it. The month is specified by a 4-bit input, $A_3:0$. For example, if the inputs are 0001, the month is January, and if the inputs are 1100, the month is December. The circuit output, Y , should be HIGH only when the month specified by the inputs has 31 days in it. Write the simplified equation, and draw the circuit diagram using a minimum number of gates. (Hint: Remember to take advantage of don't cares.).

10. Simplify the Boolean function: $F(x, y, z) = \Sigma(2, 3, 4, 5)$

11. Simplify the Boolean function: $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$

12. Simplify the following Boolean function into (a) sum-of-products form and (b) product-of-sums form:

$$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$$
13. Simplify the Boolean function $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ which has the don't-care conditions
 $d(w, x, y, z) = \Sigma(0, 2, 5)$
14. Simplify the Boolean function by finding all its prime implicants and essential prime implicants: $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$
15. Simplify the following Boolean expressions, using four-variable maps:
 (a) $A'B'C'D' + AC'D' + B'CD' + A'BCD + BC'D$ (b) $x'z + w'xy' + w(x'y + xy')$
 (c) $w'z + xz + x'y + wx'z$ (d) $AD' + B'C'D + BCD' + BC'D$
16. Simplify the following Boolean functions by first finding the prime and essential prime implicants:
 (a) $F(w, x, y, z) = \Sigma(0, 2, 5, 7, 8, 10, 12, 13, 14, 15)$
 (b) $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$
 (c) $F(A, B, C, D) = \Sigma(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$
 (d) $F(w, x, y, z) = \Sigma(0, 1, 4, 5, 6, 7, 9, 11, 14, 15)$