



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Synchronous Sequential Logic Circuits

Reetinder Sidhu

Department of Computer Science and Engineering

DIGITAL DESIGN AND COMPUTER ORGANIZATION

Synchronous Sequential Logic Circuits

Reetinder Sidhu

Department of Computer Science and
Engineering

- Digital Design
 - ▶ Combinational logic design
 - ▶ Sequential logic design
 - ★ **Synchronous Sequential Logic Circuits**
- Computer Organization
 - ▶ Architecture (microprocessor instruction set)
 - ▶ Microarchitecture (microprocessor operation)


Concepts covered

- Synchronous Sequential Logic Circuits

SYNCHRONOUS SEQUENTIAL LOGIC CIRCUITS


Potential Problems with Sequential Logic Circuits

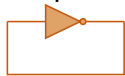- Combinational logic circuits do not contain **loops** or **cyclic paths** but sequential logic circuits do
- Loops can cause problems



- ▶ Unstable state

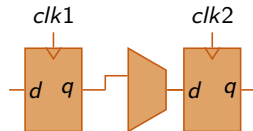
- Memory elements can suffer from **race** conditions (also called **race hazards**)




- ▶ Output depends upon input sequence

SYNCHRONOUS SEQUENTIAL LOGIC CIRCUITS

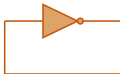- Cyclic paths are broken by inserting flip-flops in them




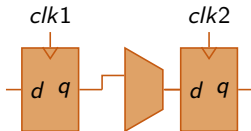- Flip-flops are synchronized by connecting them to a common clock
 - ▶ Race conditions are eliminated if the clock time period is long enough




SYNCHRONOUS SEQUENTIAL LOGIC CIRCUITS

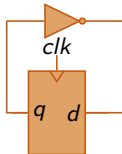- Cyclic paths are broken by inserting flip-flops in them




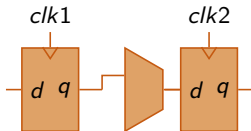- Flip-flops are synchronized by connecting them to a common clock
 - ▶ Race conditions are eliminated if the clock time period is long enough




SYNCHRONOUS SEQUENTIAL LOGIC CIRCUITS

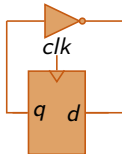- Cyclic paths are broken by inserting flip-flops in them



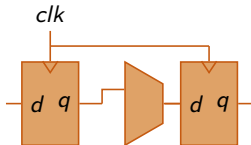- Flip-flops are synchronized by connecting them to a common clock
 - ▶ Race conditions are eliminated if the clock time period is long enough



- A **synchronous sequential logic circuit** is one in which:¹
 - ▶ Every circuit element is either a register (flip-flop) or a combinational logic circuit
 - ▶ At least one circuit element is a register
 - ▶ All registers receive the same clock signal
 - ▶ Every cyclic path contains at least one register

¹From “Digital Design and Computer Architecture 2nd Ed.”, *Harris and Harris*, ©Elsevier, 2013.

- A **synchronous sequential logic circuit** is one in which:¹
 - ▶ Every circuit element is either a register (flip-flop) or a combinational logic circuit
 - ▶ At least one circuit element is a register
 - ▶ All registers receive the same clock signal
 - ▶ Every cyclic path contains at least one register
- Only above type of sequential logic circuits studied henceforth in this course

¹From “Digital Design and Computer Architecture 2nd Ed.”, *Harris and Harris*, ©Elsevier, 2013.

- Classify the following logic circuits as combinational or synchronous sequential or neither
 - ▶ AND gate (output not connected to own input)
 - ▶ AND gate (output connected to own input)
 - ▶ D flip-flop
 - ▶ SR latch
 - ▶ Series of D flip-flops (with common clock) with output of one connected to the input of the next via an inverter