

DIGITAL DESIGN AND COMPUTER ORGANIZATION

Carry-lookahead and Prefix adders - 3

Reetinder Sidhu

Department of Computer Science and Engineering



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Carry-lookahead and Prefix adders - 3

Reetinder Sidhu

Department of Computer Science and Engineering



Course Outline




- Digital Design
 - Combinational logic design
 - Sequential logic design
 - Carry-lookahead and Prefix adders 3
- Computer Organization
 - Architecture (microprocessor instruction set)
 - Microarchitecure (microprocessor operation)


Concepts covered

Parallel Prefix Incrementer




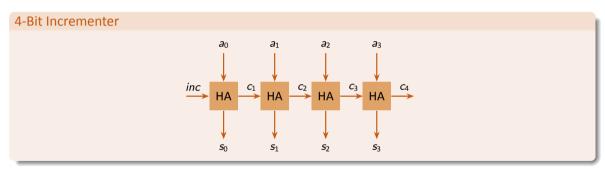




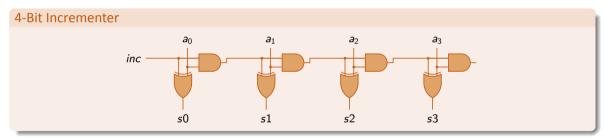



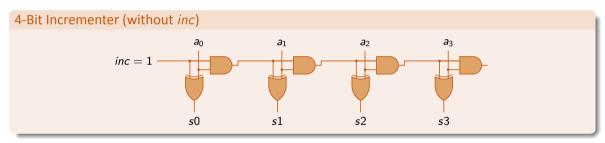




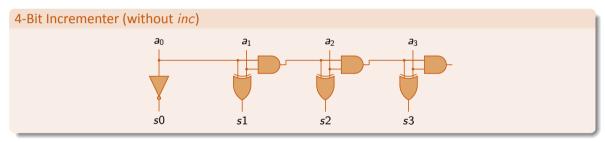

The Problem



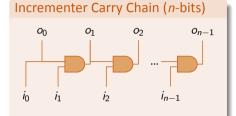


- Assuming t_g and a_g to be respectively the time and area of a two input gate, for the above carry chain:
 - Area: $(n-1)a_g$
 - ▶ Time: $(n-1)t_g$

The Problem



Incrementer Carry Chain (*n*-bits)

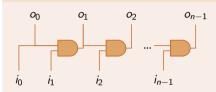

- Assuming t_g and a_g to be respectively the time and area of a two input gate, for the above carry chain:
 - Area: $(n-1)a_g$
 - ▶ Time: $(n-1)t_g$


A Prefix Problem

• Given n inputs $i_0 \ldots i_{n-1}$ and n outputs $o_0 \ldots o_{n-1}$, compute:


$$o_0 = i_0$$
 $o_1 = i_0 \cdot i_1$
 $o_2 = i_0 \cdot i_1 \cdot \cdot \cdot i_2$
 \vdots
 $o_{n-1} = i_0 \cdot i_1 \cdot \cdot \cdot \cdot i_{n-1}$

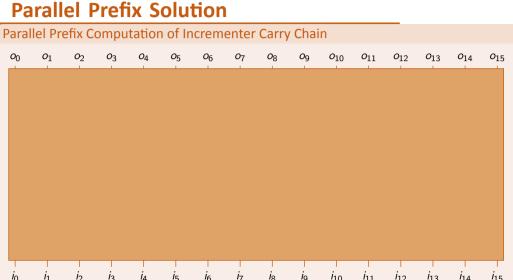- A problem of the above type where each output in a sequence is computed based on the inputs received so far (which is a prefix of the input sequence) is called a prefix problem
 - Ex: matrix multiply prefix problem









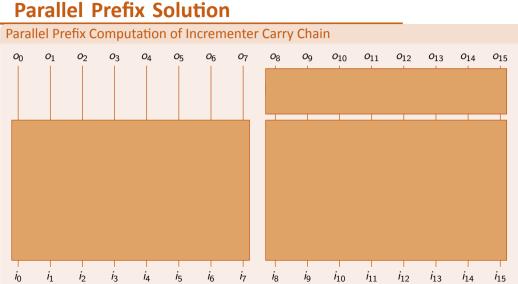




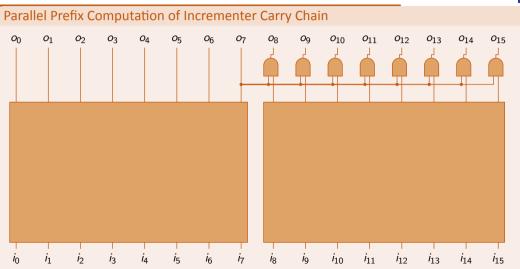




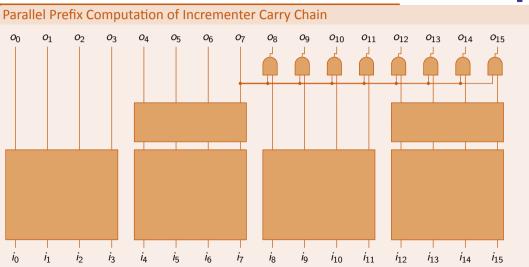




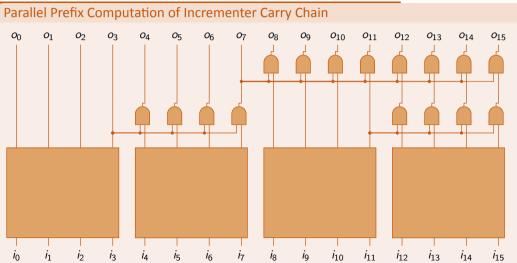




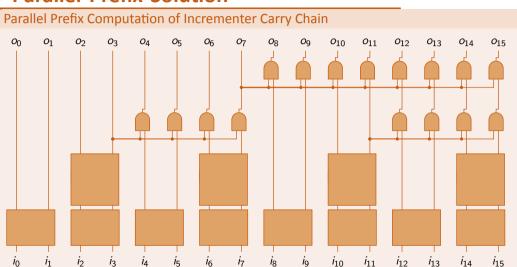




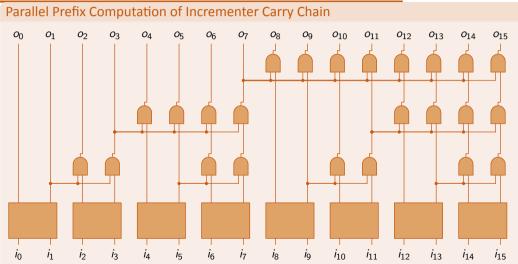




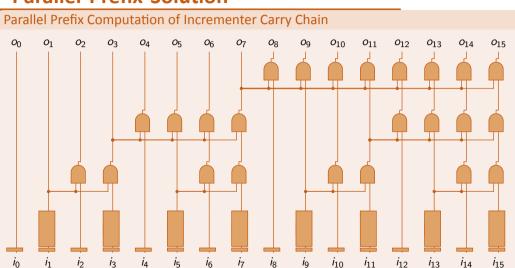




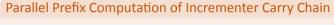


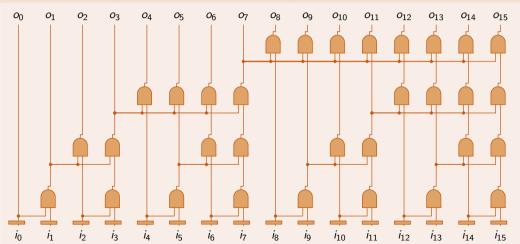




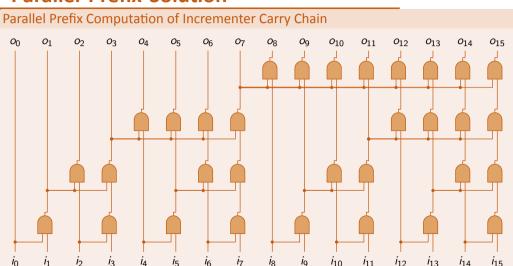




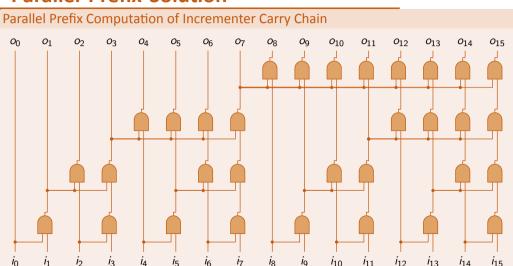




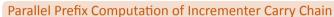


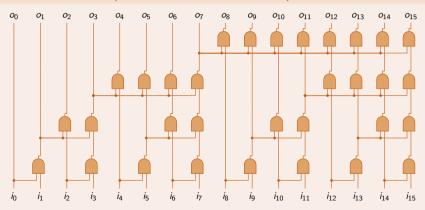

For 16 input problem:




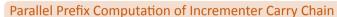


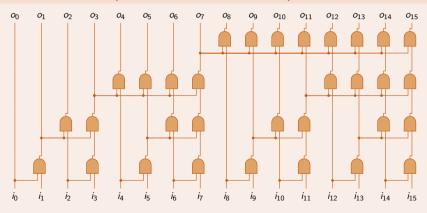

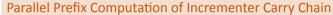- For 16 input problem:
 - ► Area: 32*a*_g






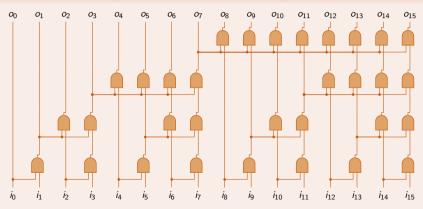

- For 16 input problem:
 - ► Area: 32*a*_g
 - ightharpoonup Time: $4t_g$



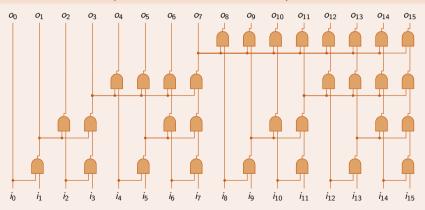
Parallel Prefix Computation of Incrementer Carry Chain



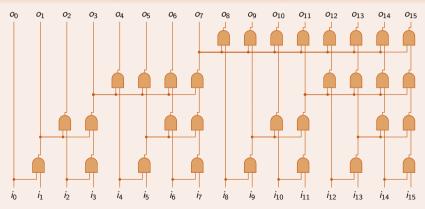- For 16 input problem:
- ► Area: 32*a*_g
- ▶ Time: $4t_g$
- For *n* input problem:









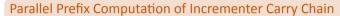- For 16 input problem:
- ► Area: 32*a*_g
- ▶ Time: $4t_g$
- For *n* input problem:
 - Area: $\frac{n}{2}(\log_2 n)a_g$






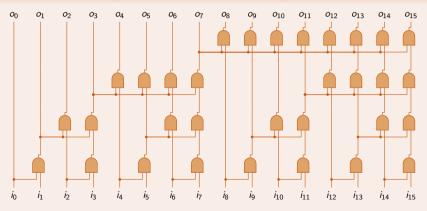

- For 16 input problem:
- ► Area: 32*a*_g
- ▶ Time: $4t_g$
- For *n* input problem:
 - ► Area: $\frac{n}{2}(\log_2 n)a_g$ ► Time: $(\log_2 n)t_g$

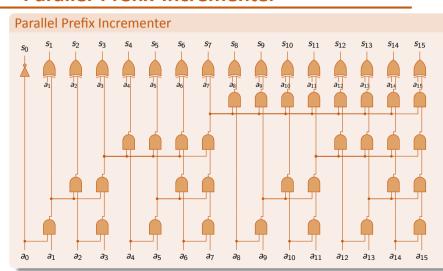CARRY-LOOKAHEAD AND PREFIX ADDERS - 3 Parallel Prefix Incrementer





Ripple Carry and Parallel Prefix Incrementer Comparison



	Area	Time
Ripple carry	$2(n-1)a_g$	$(n-1)t_g$
Parallel prefix	$\frac{n}{2}(\log_2 n)a_g + (n-1)a_g$	$(\log_2 n + 1)t_g$

CARRY-LOOKAHEAD AND PREFIX ADDERS - 3 Think About It



- Parallel prefix technique worked for AND gate
- Can it work for any gate (or Boolean function)?