



# DIGITAL DESIGN AND COMPUTER ORGANIZATION

## Adder, Subtractor, Overflow - 3

---

**Reetinder Sidhu**

Department of Computer Science and Engineering

# DIGITAL DESIGN AND COMPUTER ORGANIZATION

---

## Adder, Subtractor, Overflow - 3

**Reetinder Sidhu**

Department of Computer Science and  
Engineering

- Digital Design
  - ▶ Combinational logic design
    - ★ **Adder, Subtractor, Overflow - 3**
  - ▶ Sequential logic design
- Computer Organization
  - ▶ Architecture (microprocessor instruction set)
  - ▶ Microarchitecture (microprocessor operation)

### Concepts covered

- Logic Circuits for:
  - ▶ Increment
  - ▶ Two's Complement
  - ▶ Subtractor
  - ▶ Adder / Subtractor

# ADDER, SUBTRACTOR, OVERFLOW - 3


## Increment Logic Circuit

---

# ADDER, SUBTRACTOR, OVERFLOW - 3

## Increment Logic Circuit


### 4-bit Ripple Carry Adder

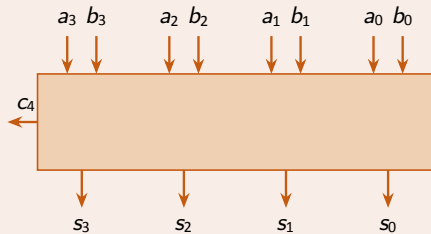

# ADDER, SUBTRACTOR, OVERFLOW - 3

## Increment Logic Circuit


### 4-bit Ripple Carry Adder

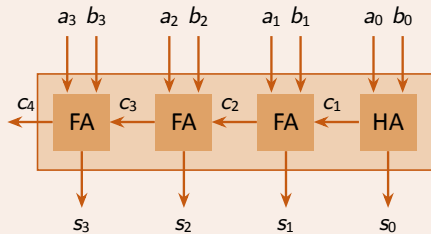

# ADDER, SUBTRACTOR, OVERFLOW - 3

## Increment Logic Circuit

### 4-bit Ripple Carry Adder

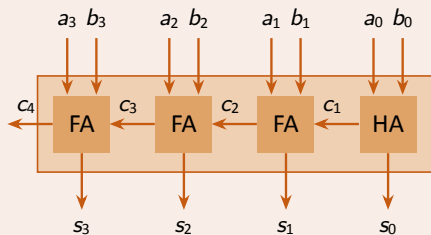


- Carry “ripples” through the carry chain

# ADDER, SUBTRACTOR, OVERFLOW - 3

## Increment Logic Circuit


### 4-bit Ripple Carry Adder

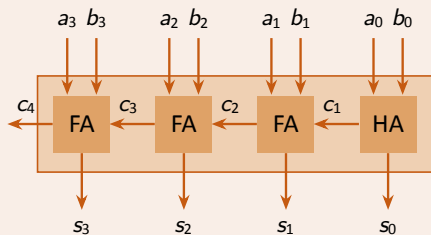

- Carry “ripples” through the carry chain

### Incrementer Logic Circuit

- Add 1 to input number

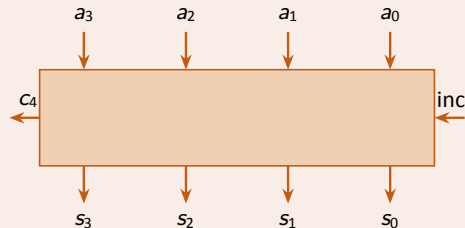




# ADDER, SUBTRACTOR, OVERFLOW - 3

## Increment Logic Circuit


### 4-bit Ripple Carry Adder

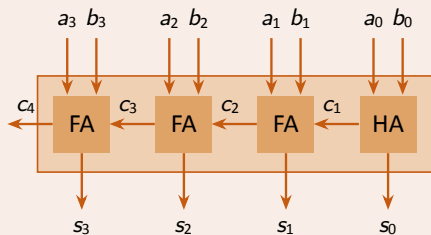

- Carry “ripples” through the carry chain

### Incrementer Logic Circuit


- Add 1 to input number

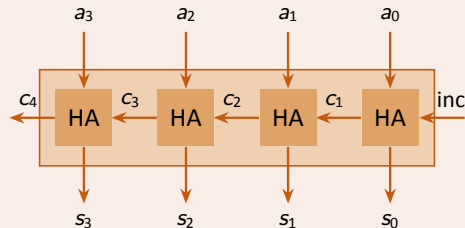

# ADDER, SUBTRACTOR, OVERFLOW - 3

## Increment Logic Circuit


### 4-bit Ripple Carry Adder

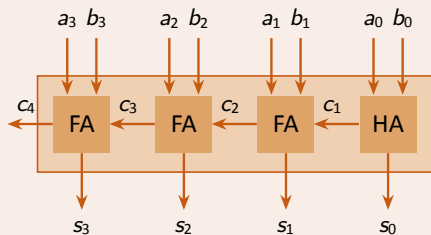

- Carry “ripples” through the carry chain

### Incrementer Logic Circuit

- Add 1 to input number

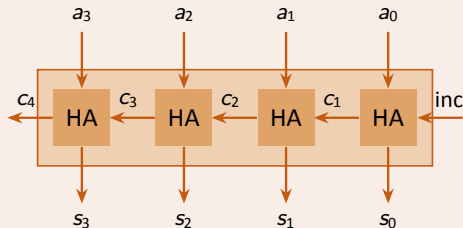


- Less logic resources than ripple carry adder

### Two's Complement Subtractor

- Subtract one four bit number ( $b_3b_2b_1b_0$ ) from another ( $a_3a_2a_1a_0$ )
- Take two's complement of  $b_3b_2b_1b_0$ :
  - ▶ Invert  $b_3b_2b_1b_0$
  - ▶ Add one to it
- Add above number to  $a_3a_2a_1a_0$  yielding result

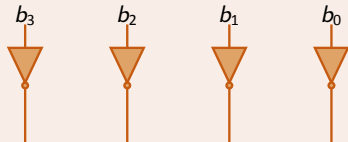
### Two's Complement Subtractor

- Subtract one four bit number ( $b_3 b_2 b_1 b_0$ ) from another ( $a_3 a_2 a_1 a_0$ )
- Take two's complement of  $b_3 b_2 b_1 b_0$ :
  - ▶ Invert  $b_3 b_2 b_1 b_0$
  - ▶ Add one to it
- Add above number to  $a_3 a_2 a_1 a_0$  yielding result


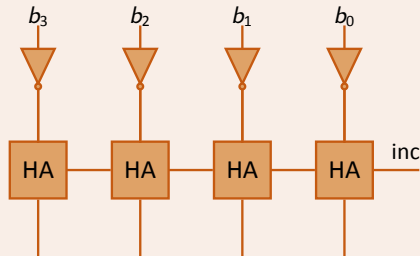
### Two's Complement Subtractor

- Subtract one four bit number ( $b_3 b_2 b_1 b_0$ ) from another ( $a_3 a_2 a_1 a_0$ )
- Take two's complement of  $b_3 b_2 b_1 b_0$ :
  - ▶ Invert  $b_3 b_2 b_1 b_0$
  - ▶ Add one to it
- Add above number to  $a_3 a_2 a_1 a_0$  yielding result




# ADDER, SUBTRACTOR, OVERFLOW - 3

## Two's Complement Subtractor
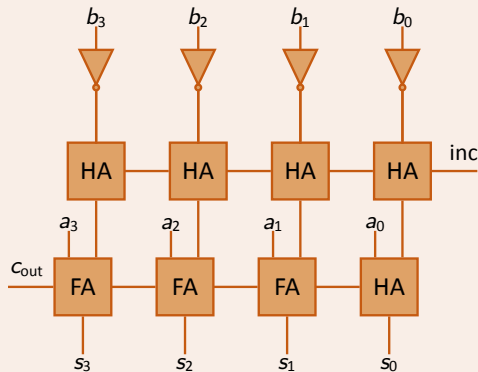
### Two's Complement Subtractor

- Subtract one four bit number ( $b_3 b_2 b_1 b_0$ ) from another ( $a_3 a_2 a_1 a_0$ )
- Take two's complement of  $b_3 b_2 b_1 b_0$ :
  - ▶ Invert  $b_3 b_2 b_1 b_0$
  - ▶ Add one to it
- Add above number to  $a_3 a_2 a_1 a_0$  yielding result



# ADDER, SUBTRACTOR, OVERFLOW - 3

## Two's Complement Adder / Subtractor

### XOR as Controlled Inverter

- Truth table:

<i>inv</i>	<i>a</i>	<i>y</i>
0	0	0
0	1	1
1	0	1
1	1	0

- Symbol:



- When  $inv = 0$ ,  $y = a$
- When  $inv = 1$ ,  $y = \bar{a}$

# ADDER, SUBTRACTOR, OVERFLOW - 3

## Two's Complement Adder / Subtractor

### XOR as Controlled Inverter

- Truth table:


inv	a	y
0	0	0
0	1	1
1	0	1
1	1	0

- Symbol:



- When  $inv = 0$ ,  $y = a$
- When  $inv = 1$ ,  $y = \bar{a}$

### Two's Complement Adder / Subtractor

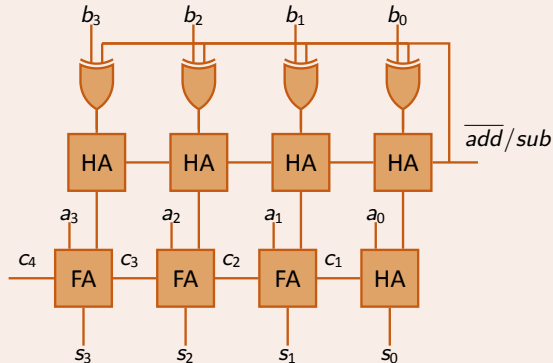


- $\overline{add/sub}$  denotes:
  - ▶ Addition when  $\overline{add/sub} = 0$
  - ▶ Subtraction when  $\overline{add/sub} = 1$



# ADDER, SUBTRACTOR, OVERFLOW - 3

## Think About It

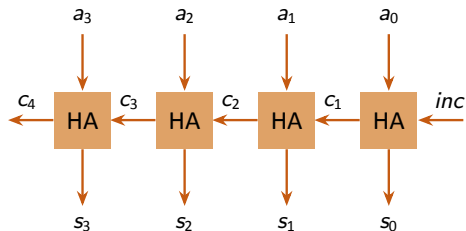

- Above logic circuit increments only when  $inc = 1$
- Construct a logic circuit which always increments (so no  $inc$  input)
- Construct a decrementer logic circuit