
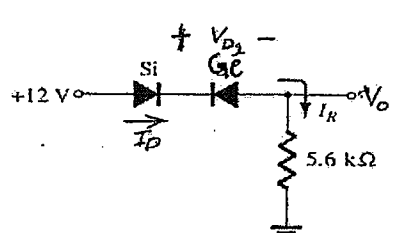


**MAY 2017: END SEMESTER ASSESSMENT (ESA) B.TECH. II SEMESTER**  
**UE16EC 101- BASIC ELECTRONICS**


Time: 3 Hrs		Answer All Questions	Max Marks: 100
1	a)	Name the 3 types of resistances associated with the diode? Derive the expression for the dynamic resistance of the diode.	6
	b)	The reverse saturation current of a Si diode is 5 nA at a temperature of 300K. Find the diode current and its dynamic resistance at 60°C and $V_D = 0.5$ V.	4
	c)	With a neat diagram, explain the basic construction and working of an LED. Why is called IR LED? Justify. Given Energy gap for Ga As = 1.43 eV.	6
	d)	Determine $I_D$ , $V_{D2}$ , and $V_O$ for the circuit shown.	4
			
2	a)	With neat Circuit diagram and waveforms explain the working of bridge rectifier. Write the expression for the output dc voltage $V_{dc}$ and PIV rating of the diode.	8
	b)	Draw the circuit diagram of a center tapped FWR with capacitor filter. Calculate the percentage ripple for the voltage developed across a 120 μF filter capacitor when providing a load current of 80 mA. The full wave rectifier operating from 60 Hz supply develops a peak rectified voltage of 25 V.	7
	c)	Design a zener regulator that will maintain the output voltage at 20 V across a 1 KΩ resistor. Input varies between 30 V to 50 V. Find $R_S$ and $I_{Z\max}$ .	5
3	a)	Simplify the following Boolean expression and realize the simplified expression using NOR gates. $Y = (\overline{A} \overline{C} + \overline{B} C) (\overline{A} \overline{B} + \overline{A} B \overline{C})$	5
	b)	Draw the circuit diagram of a Full-Adder using NAND gates. Write its output equations and its truth table.	5
	c)	Draw the logic diagram and the truth table of a clocked RS flip-flop. How to convert the same into a clocked D flip-flop and what is the advantage of it?	6
	d)	Realize a 3-input XOR gate using 4-to-1 MUX.	4
4	a)	Draw the output characteristics of CB configuration marking 3 regions of operation. State the biasing conditions for these regions and explain behavior of transistor in these regions along with the output current equation for active region.	9

- 7

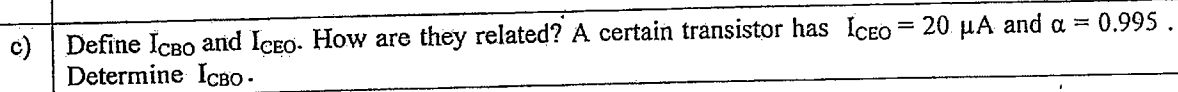

- 6.

- 8.

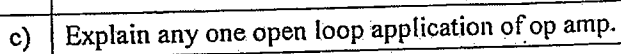

- |    |  |
|----|--|
| c) | Explain any one open loop application of op amp. |
|----|--|