



# DIGITAL DESIGN AND COMPUTER ORGANIZATION

## Carry-lookahead and Prefix adders - 2

---

**Reetinder Sidhu**

Department of Computer Science and Engineering

# DIGITAL DESIGN AND COMPUTER ORGANIZATION

---

## Carry-lookahead and Prefix adders - 2

**Reetinder Sidhu**

Department of Computer Science and  
Engineering

- Digital Design
  - ▶ Combinational logic design
  - ▶ Sequential logic design
    - ★ Carry-lookahead and Prefix adders - 2
- Computer Organization
  - ▶ Architecture (microprocessor instruction set)
  - ▶ Microarchitecture (microprocessor operation)

### Concepts covered

- Carry-Lookahead Adder

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2

## Scaling Carry-Lookahead Adders

---

- Ripple carry adders are compact but slow
- Carry-lookahead adders are fast enough but difficult to scale to large sizes

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2

## Scaling Carry-Lookahead Adders


---

- Ripple carry adders are compact but slow
- Carry-lookahead adders are fast enough but difficult to scale to large sizes
- One solution is a hybrid approach:
  - ▶ Split the adder into a number of blocks
  - ▶ Use carry-lookahead technique to add bits in each block
  - ▶ Combine the blocks together using ripple carry technique

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
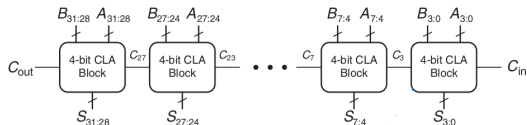
## Approach

- Carry-lookahead for blocks which are combined using ripple carry technique:




Source: Elsevier

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
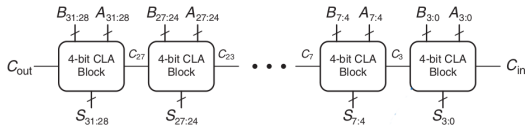
## Approach

- Carry-lookahead for blocks which are combined using ripple carry technique:




Source: Elsevier

- Each 4-bit block can be a carry-lookahead adder

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
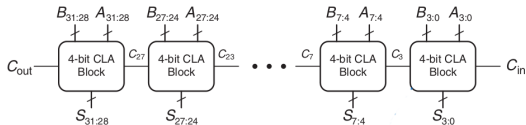
## Approach

- Carry-lookahead for blocks which are combined using ripple carry technique:



Source: Elsevier


- Each 4-bit block can be a carry-lookahead adder
- Critical path is from  $a_0$ ,  $b_0$  and  $c_{in}$  to  $s_{31}$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
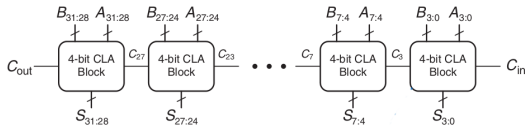
## Approach

- Carry-lookahead for blocks which are combined using ripple carry technique:




Source: Elsevier

- Each 4-bit block can be a carry-lookahead adder
- Critical path is from  $a_0$ ,  $b_0$  and  $c_{in}$  to  $s_{31}$
- So it is important to compute  $c_3$ ,  $c_7$ , ...,  $c_{27}$  quickly

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
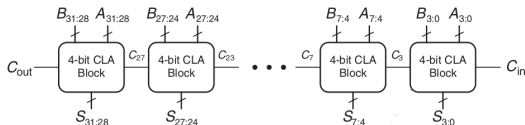
## Approach

- Carry-lookahead for blocks which are combined using ripple carry technique:




Source: Elsevier

- Each 4-bit block can be a carry-lookahead adder
- Critical path is from  $a_0$ ,  $b_0$  and  $c_{in}$  to  $s_{31}$
- So it is important to compute  $c_3$ ,  $c_7$ ,  $\dots$ ,  $c_{27}$  quickly
- Not so important to compute sum outputs  $s_0$  to  $s_{30}$  quickly

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
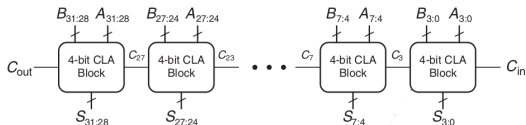
## Approach

- Carry-lookahead for blocks which are combined using ripple carry technique:




Source: Elsevier

- Each 4-bit block can be a carry-lookahead adder
- Critical path is from  $a_0$ ,  $b_0$  and  $c_{in}$  to  $s_{31}$
- So it is important to compute  $c_3$ ,  $c_7$ ,  $\dots$ ,  $c_{27}$  quickly
  - So use carry lookahead approach to compute above carry values
- Not so important to compute sum outputs  $s_0$  to  $s_{30}$  quickly

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
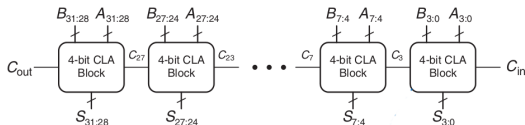
## Approach

- Carry-lookahead for blocks which are combined using ripple carry technique:




Source: Elsevier

- Each 4-bit block can be a carry-lookahead adder
- Critical path is from  $a_0$ ,  $b_0$  and  $c_{in}$  to  $s_{31}$
- So it is important to compute  $c_3$ ,  $c_7$ ,  $\dots$ ,  $c_{27}$  quickly
  - So use carry lookahead approach to compute above carry values
- Not so important to compute sum outputs  $s_0$  to  $s_{30}$  quickly
  - So use ripple carry technique inside each block as well to compute the sum outputs

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
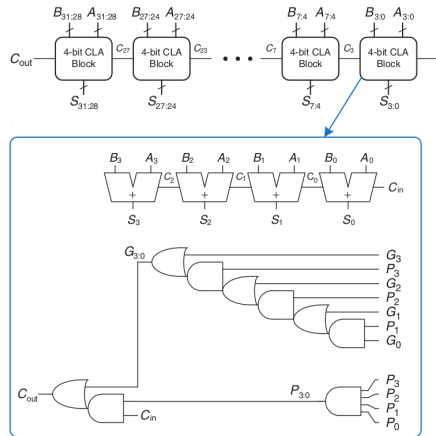
## Block structure


- $$C_{out} = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0C_{in}$$
$$= g_3 + p_3(g_2 + p_2g_1 + p_2p_1g_0) + p_3p_2p_1p_0C_{in}$$
$$= g_3 + p_3(g_2 + p_2(g_1 + p_1g_0)) + p_3p_2p_1p_0C_{in}$$
- Logic circuit for above Boolean formula shown in figure



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
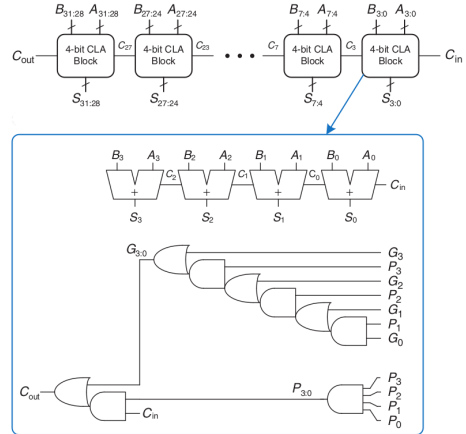
## Critical Path Delay


- Critical path is from  $a_0, b_0$  and  $c_{in}$  to  $s_{31}$
- Three parts of the critical path delay are the time required to:
  - ▶ compute various  $p$  and  $g$
  - ▶ for carry to propagate from  $c_0$  to  $c_{27}$
  - ▶ compute sum  $s_{31}$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
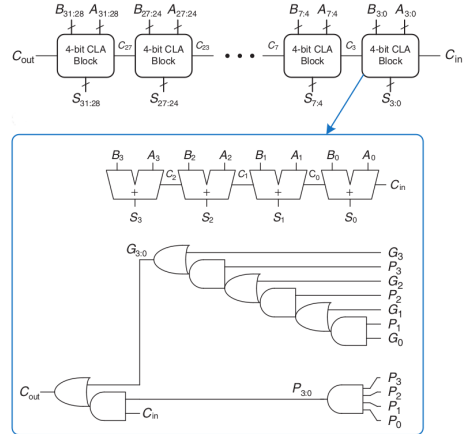
## Critical Path Delay


- Time required to compute various  $p$  and  $g$ :
  - Compute  $p_i$  and  $g_i$  ( $0 \leq i < 4$ ) in each block in time  $t_{pg}$
  - Compute  $g_{3:0}$  in each block in time  $t_{pg\_block}$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
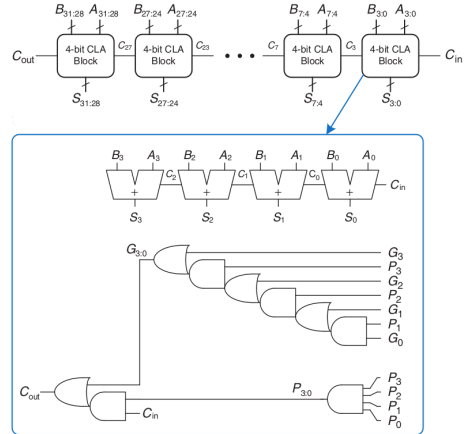
## Critical Path Delay

- Time required for carry to propagate from  $c_0$  to  $c_{27}$ :
  - In each block,  $c_{in}$  propagates through an AND gate and an OR gate to emerge as  $c_{out}$  in time  $t_{AND\_OR}$
  - Since carry propagates in above manner through first seven blocks, time required is  $7t_{AND\_OR}$






# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2
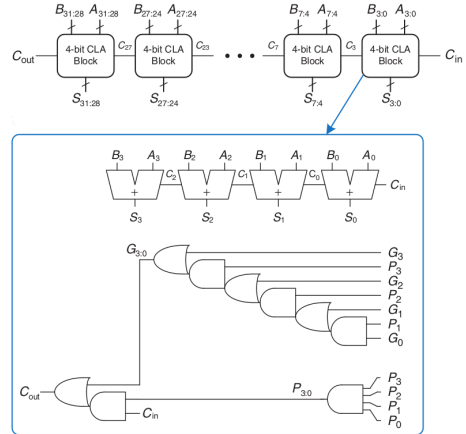
## Critical Path Delay

- Time required to compute sum  $s_{31}$ :
  - Once  $c_{27}$  is available, it needs to propagate through the four full adders, each of which takes time  $t_{FA}$
  - So total time required is  $4t_{FA}$
- So critical path delay is:
  - $t_{CLA} = t_{pg} + t_{pg\_block} + 7t_{AND\_OR} + 4t_{FA}$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 2

## Critical Path Delay

- Generalizing, if we assume an  $N$ -bit adder is constructed using  $k$ -bit blocks:

- ▶  $\frac{N}{k}$  blocks each if size  $k$  will be used
- ▶ Hence critical path delay would be:

$$t_{CLA} =$$

$$t_{pg} + t_{pg\_block} + \left(\frac{N}{k} - 1\right)t_{AND\_OR} + kt_{FA}$$

