



# DIGITAL DESIGN AND COMPUTER ORGANIZATION

## Carry-lookahead and Prefix adders - 1

---

**Reetinder Sidhu**

Department of Computer Science and Engineering

# DIGITAL DESIGN AND COMPUTER ORGANIZATION

---

## Carry-lookahead and Prefix adders - 1

**Reetinder Sidhu**

Department of Computer Science and  
Engineering

- Digital Design
  - ▶ Combinational logic design
  - ▶ Sequential logic design
    - ★ Carry-lookahead and Prefix adders - 1
- Computer Organization
  - ▶ Architecture (microprocessor instruction set)
  - ▶ Microarchitecture (microprocessor operation)


### Concepts covered

- Adder Performance Evaluation
- Carry-Lookahead Adder

- We evaluate the performance of various adder types by estimating their area and time requirements
  - ▶ Area is estimated by number of logic gates required
  - ▶ Time is estimated based on critical path delay
- We assume that all two input AND, OR and XOR gates:
  - ▶ Occupy area  $a_g$
  - ▶ Have a propagation delay  $t_g$
  - ▶ Somewhat simplifying, but realistic assumption
- How about gates with more than two inputs? For a  $k$ -input AND/OR/XOR gate:
  - ▶ Its area is estimated to be  $(k - 1)a_g$ 
    - ★ Since a  $k$  input AND/OR/XOR can be constructed using  $k - 1$  two input gates of the type
  - ▶ Its propagation delay is estimated to be  $\lceil \log_2 k \rceil t_d$ 
    - ★ Shortest delay above obtained when the  $k - 1$  gates are arranged in a “tree-like” fashion
- No inverters in adder designs considered
  - ▶ If present, can be ignored in initial analysis

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Ripple Carry Adder Area and Time

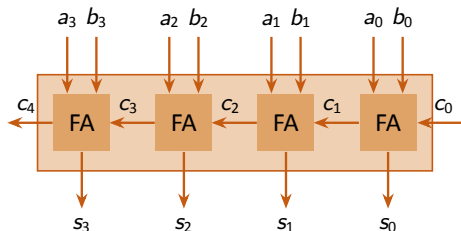

- Area requirements:

- ▶ Each full adder contains five two input gates (for carry) and one three input gate (for sum)
- ▶ So each full adder occupies  $7a_g$  area

- An  $n$ -bit ripple carry adder thus occupies  $7na_g$  area

- Time requirements: For an  $n$ -bit ripple carry adder, critical path delay is composed of:

- ▶ Propagation delay from  $c_0$  to  $c_{n-1}$ 
  - ★ Signal passes through two gates in each of the  $n - 1$  stages
  - ★  $2(n - 1)t_g$  time required
- ▶ Sum computation
  - ★  $2t_g$  time required for three input XOR gate

- An  $n$ -bit ripple carry adder thus occupies  $2nt_g$  time

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## The Carry Chain Problem


---

- Time requirement for addition increases linearly with number of bits to be added
  - ▶ If 16-bit addition requires  $x$  time, 64-bit addition will require  $4x$  time
- Same for subtraction, increment and decrement
- For such a fundamental operation faster solutions are required
- Speed can be improved by eliminating the carry chain

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
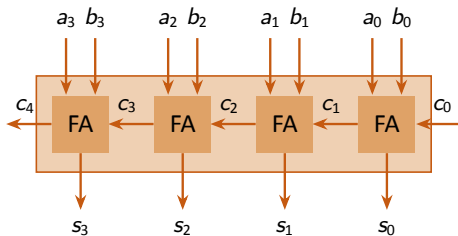
## Direct generation of carry?

- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):




# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Direct generation of carry?

- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):

- ▶  $c_1 = a_0 b_0 + b_0 c_0 + c_0 a_0$

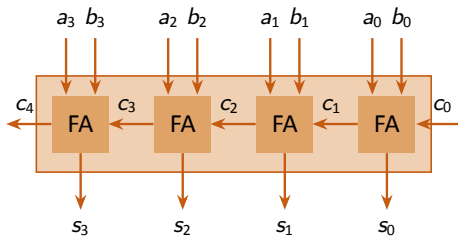




# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
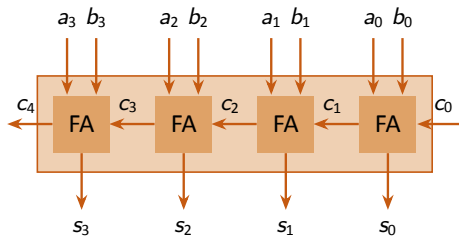
## Direct generation of carry?

- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):

- ▶  $c_1 = a_0b_0 + b_0c_0 + c_0a_0 = a_0b_0 + (a_0 + b_0)c_0$




# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
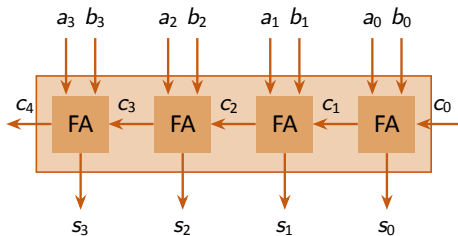
## Direct generation of carry?

- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):

- ▶  $c_1 = a_0b_0 + b_0c_0 + c_0a_0 = a_0b_0 + (a_0 + b_0)c_0$
- ▶  $c_2 = a_1b_1 + (a_1 + b_1)c_1$




# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
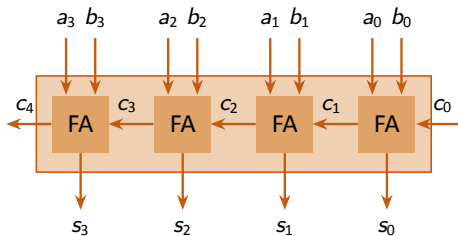
## Direct generation of carry?

- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):

- ▶  $c_1 = a_0 b_0 + b_0 c_0 + c_0 a_0 = a_0 b_0 + (a_0 + b_0) c_0$
- ▶  $c_2 = a_1 b_1 + (a_1 + b_1) c_1$   
 $= a_1 b_1 + (a_1 + b_1)(a_0 b_0 + (a_0 + b_0) c_0)$




# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Direct generation of carry?

- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):

- ▶  $c_1 = a_0 b_0 + b_0 c_0 + c_0 a_0 = a_0 b_0 + (a_0 + b_0) c_0$

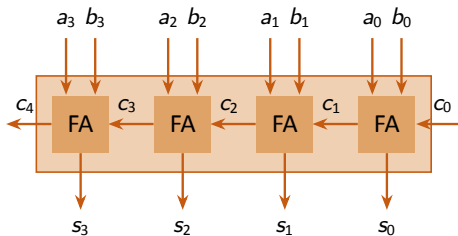
- ▶  $c_2 = a_1 b_1 + (a_1 + b_1) c_1$   
 $= a_1 b_1 + (a_1 + b_1)(a_0 b_0 + (a_0 + b_0) c_0)$   
 $= a_1 b_1 + (a_1 + b_1) a_0 b_0 + (a_1 + b_1)(a_0 + b_0) c_0$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
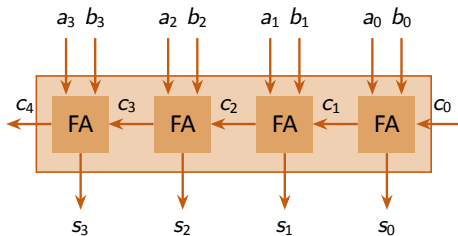
## Direct generation of carry?


- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):
  - ▶  $c_1 = a_0b_0 + b_0c_0 + c_0a_0 = a_0b_0 + (a_0 + b_0)c_0$
  - ▶  $c_2 = a_1b_1 + (a_1 + b_1)c_1$   
 $= a_1b_1 + (a_1 + b_1)(a_0b_0 + (a_0 + b_0)c_0)$   
 $= a_1b_1 + (a_1 + b_1)a_0b_0 + (a_1 + b_1)(a_0 + b_0)c_0$
- Lots of terms of type  $a_ib_i$  and  $(a_i + b_i)$ . So to make the formulas simpler, we substitute:



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
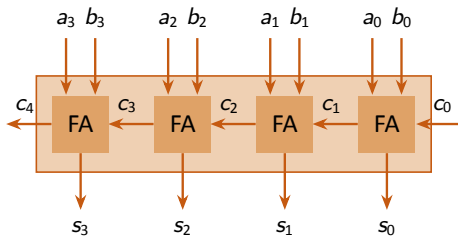
## Direct generation of carry?


- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):
  - ▶  $c_1 = a_0b_0 + b_0c_0 + c_0a_0 = a_0b_0 + (a_0 + b_0)c_0$
  - ▶  $c_2 = a_1b_1 + (a_1 + b_1)c_1$   
 $= a_1b_1 + (a_1 + b_1)(a_0b_0 + (a_0 + b_0)c_0)$   
 $= a_1b_1 + (a_1 + b_1)a_0b_0 + (a_1 + b_1)(a_0 + b_0)c_0$
- Lots of terms of type  $a_ib_i$  and  $(a_i + b_i)$ . So to make the formulas simpler, we substitute:
  - ▶  $g_i = a_ib_i$
  - ▶  $p_i = a_i + b_i$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
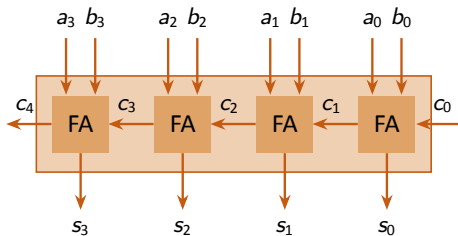
## Direct generation of carry?


- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):
  - ▶  $c_1 = a_0b_0 + b_0c_0 + c_0a_0 = a_0b_0 + (a_0 + b_0)c_0$
  - ▶  $c_2 = a_1b_1 + (a_1 + b_1)c_1$   
 $= a_1b_1 + (a_1 + b_1)(a_0b_0 + (a_0 + b_0)c_0)$   
 $= a_1b_1 + (a_1 + b_1)a_0b_0 + (a_1 + b_1)(a_0 + b_0)c_0$
- Lots of terms of type  $a_ib_i$  and  $(a_i + b_i)$ . So to make the formulas simpler, we substitute:
  - ▶  $g_i = a_ib_i$
  - ▶  $p_i = a_i + b_i$
- Above substitution yields:
  - ▶  $c_1 = g_0 + p_0c_0$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
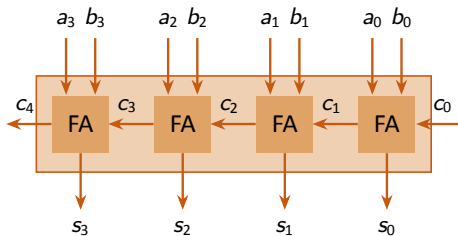
## Direct generation of carry?

- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):
  - ▶  $c_1 = a_0b_0 + b_0c_0 + c_0a_0 = a_0b_0 + (a_0 + b_0)c_0$
  - ▶  $c_2 = a_1b_1 + (a_1 + b_1)c_1$   
 $= a_1b_1 + (a_1 + b_1)(a_0b_0 + (a_0 + b_0)c_0)$   
 $= a_1b_1 + (a_1 + b_1)a_0b_0 + (a_1 + b_1)(a_0 + b_0)c_0$
- Lots of terms of type  $a_ib_i$  and  $(a_i + b_i)$ . So to make the formulas simpler, we substitute:
  - ▶  $g_i = a_ib_i$
  - ▶  $p_i = a_i + b_i$
- Above substitution yields:
  - ▶  $c_1 = g_0 + p_0c_0$
  - ▶  $c_2 = g_1 + p_1g_0 + p_1p_0c_0$






# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
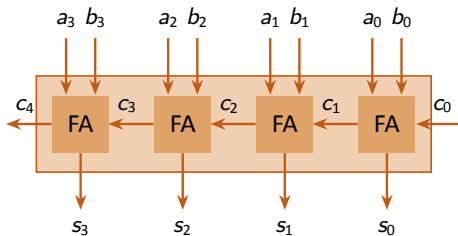
## Direct generation of carry?


- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):
  - ▶  $c_1 = a_0 b_0 + b_0 c_0 + c_0 a_0 = a_0 b_0 + (a_0 + b_0) c_0$
  - ▶  $c_2 = a_1 b_1 + (a_1 + b_1) c_1$   
 $= a_1 b_1 + (a_1 + b_1)(a_0 b_0 + (a_0 + b_0) c_0)$   
 $= a_1 b_1 + (a_1 + b_1) a_0 b_0 + (a_1 + b_1)(a_0 + b_0) c_0$
- Lots of terms of type  $a_i b_i$  and  $(a_i + b_i)$ . So to make the formulas simpler, we substitute:
  - ▶  $g_i = a_i b_i$
  - ▶  $p_i = a_i + b_i$
- Above substitution yields:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1
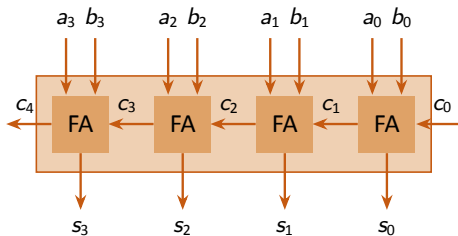
## Direct generation of carry?


- Compute carry ( $c_i$ ) directly from inputs ( $a_i$  and  $b_i$ ):
  - ▶  $c_1 = a_0 b_0 + b_0 c_0 + c_0 a_0 = a_0 b_0 + (a_0 + b_0) c_0$
  - ▶  $c_2 = a_1 b_1 + (a_1 + b_1) c_1$   
 $= a_1 b_1 + (a_1 + b_1)(a_0 b_0 + (a_0 + b_0) c_0)$   
 $= a_1 b_1 + (a_1 + b_1) a_0 b_0 + (a_1 + b_1)(a_0 + b_0) c_0$
- Lots of terms of type  $a_i b_i$  and  $(a_i + b_i)$ . So to make the formulas simpler, we substitute:
  - ▶  $g_i = a_i b_i$
  - ▶  $p_i = a_i + b_i$
- Above substitution yields:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## 4-bit Carry-Lookahead Adder

### 4-bit Carry-Lookahead Adder

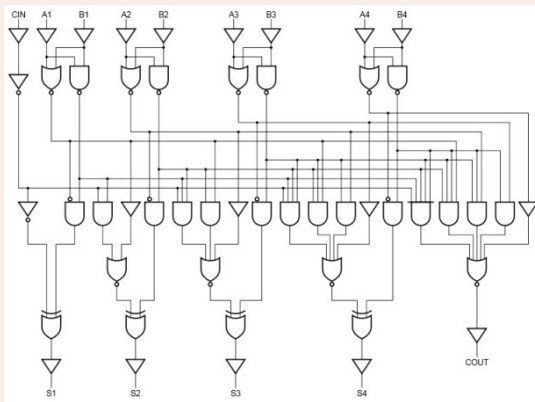

Source: *electronics*hub

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Area Estimate

---

- All gates mentioned below are two input gates
- From the carry formulas, we see that for a carry-lookahead adder:

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Area Estimate

---

- All gates mentioned below are two input gates
- From the carry formulas, we see that for a carry-lookahead adder:
  - ▶ For  $c_1$  4 gates are required

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Area Estimate

---

- All gates mentioned below are two input gates
- From the carry formulas, we see that for a carry-lookahead adder:
  - ▶ For  $c_1$  4 gates are required
  - ▶ For  $c_i$  number of gates required is  $2i + 2$  greater than gates required for  $c_{i-1}$

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Area Estimate

---

- All gates mentioned below are two input gates
- From the carry formulas, we see that for a carry-lookahead adder:
  - ▶ For  $c_1$  4 gates are required
  - ▶ For  $c_i$  number of gates required is  $2i + 2$  greater than gates required for  $c_{i-1}$
  - ▶ So  $i(i + 3)$  gates are required for  $c_1$  to  $c_i$

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Area Estimate

---

- All gates mentioned below are two input gates
- From the carry formulas, we see that for a carry-lookahead adder:
  - ▶ For  $c_1$  4 gates are required
  - ▶ For  $c_i$  number of gates required is  $2i + 2$  greater than gates required for  $c_{i-1}$
  - ▶ So  $i(i + 3)$  gates are required for  $c_1$  to  $c_i$
  - ▶ Each three input XOR gate (for sum) would count as two gates



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Area Estimate

---

- All gates mentioned below are two input gates
- From the carry formulas, we see that for a carry-lookahead adder:
  - ▶ For  $c_1$  4 gates are required
  - ▶ For  $c_i$  number of gates required is  $2i + 2$  greater than gates required for  $c_{i-1}$
  - ▶ So  $i(i + 3)$  gates are required for  $c_1$  to  $c_i$
  - ▶ Each three input XOR gate (for sum) would count as two gates
- So an  $n$ -bit carry-lookahead adder would require  $n^2 + 5n$  gates

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$
- Critical path delay for a carry-lookahead adder is composed of:

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$
- Critical path delay for a carry-lookahead adder is composed of:
  - ▶  $p$  and  $g$  computation
    - ★  $t_g$  time required required for two input AND/OR gate

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$
- Critical path delay for a carry-lookahead adder is composed of:
  - ▶  $p$  and  $g$  computation
    - ★  $t_g$  time required required for two input AND/OR gate
  - ▶ carry computation delay
    - ★ time required for  $c_i$  depends on  $i$

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$
- Critical path delay for a carry-lookahead adder is composed of:
  - ▶  $p$  and  $g$  computation
    - ★  $t_g$  time required required for two input AND/OR gate
  - ▶ carry computation delay
    - ★ time required for  $c_i$  depends on  $i$
  - ▶ sum computation
    - ★  $2t_g$  time required for three input XOR

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$
- Critical path delay for a carry-lookahead adder is composed of:
  - ▶  $p$  and  $g$  computation
    - ★  $t_g$  time required required for two input AND/OR gate
  - ▶ carry computation delay
    - ★ time required for  $c_i$  depends on  $i$
  - ▶ sum computation
    - ★  $2t_g$  time required for three input XOR
- Carry computation delay: for an  $n$ -bit carry-lookahead adder, longest delay is for  $c_{n-1}$ , which is composed of:

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$
- Critical path delay for a carry-lookahead adder is composed of:
  - ▶  $p$  and  $g$  computation
    - ★  $t_g$  time required required for two input AND/OR gate
  - ▶ carry computation delay
    - ★ time required for  $c_i$  depends on  $i$
  - ▶ sum computation
    - ★  $2t_g$  time required for three input XOR
- Carry computation delay: for an  $n$ -bit carry-lookahead adder, longest delay is for  $c_{n-1}$ , which is composed of:
  - ▶ Delay for the minterm  $p_{n-2} p_{n-3} \dots p_0 c_0$ 
    - ★  $n$  input AND gate requires  $\lceil \log_2(n-1) \rceil t_g$  time



# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$
- Critical path delay for a carry-lookahead adder is composed of:
  - ▶  $p$  and  $g$  computation
    - ★  $t_g$  time required required for two input AND/OR gate
  - ▶ carry computation delay
    - ★ time required for  $c_i$  depends on  $i$
  - ▶ sum computation
    - ★  $2t_g$  time required for three input XOR
- Carry computation delay: for an  $n$ -bit carry-lookahead adder, longest delay is for  $c_{n-1}$ , which is composed of:
  - ▶ Delay for the minterm  $p_{n-2} p_{n-3} \dots p_0 c_0$ 
    - ★  $n$  input AND gate requires  $\lceil \log_2(n-1) \rceil t_g$  time
  - ▶ Delay for the OR of all minterms
    - ★ OR of  $n$  inputs requires  $\lceil \log_2(n-1) \rceil t_g$  time

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Carry-Lookahead Adder Time Estimate

- Carry formulas for 4-bit carry-lookahead adder:
  - ▶  $c_1 = g_0 + p_0 c_0$
  - ▶  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
  - ▶  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
  - ▶  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$
- Critical path delay for a carry-lookahead adder is composed of:
  - ▶  $p$  and  $g$  computation
    - ★  $t_g$  time required required for two input AND/OR gate
  - ▶ carry computation delay
    - ★ time required for  $c_i$  depends on  $i$
  - ▶ sum computation
    - ★  $2t_g$  time required for three input XOR
- Carry computation delay: for an  $n$ -bit carry-lookahead adder, longest delay is for  $c_{n-1}$ , which is composed of:
  - ▶ Delay for the minterm  $p_{n-2} p_{n-3} \dots p_0 c_0$ 
    - ★  $n$  input AND gate requires  $\lceil \log_2(n-1) \rceil t_g$  time
  - ▶ Delay for the OR of all minterms
    - ★ OR of  $n$  inputs requires  $\lceil \log_2(n-1) \rceil t_g$  time
- So total time required (critical path delay) for an  $n$ -bit carry-lookahead adder:  
 $2\lceil \log_2(n-1) \rceil t_g + 3t_g$

# CARRY-LOOKAHEAD AND PREFIX ADDERS - 1

## Performance Comparison

- Area and time estimates for  $n$ -bit adders:

	Area	Time
Ripple carry	$7na_g$	$2nt_g$
Carry-lookahead	$(n^2 + 5n)a_g$	$2\lceil \log_2(n-1) \rceil t_g + 3t_g$

- Compared to the ripple carry adder's linear delay increase with size, the carry-lookahead adder delay increase only logarithmically, resulting in dramatically faster adders
- However, the area of the carry-lookahead adder increase quadratically with size
- Is there an adder design that retains the carry-lookahead adder's speed but has significantly lesser area?